



New
Mansoura
University


جامعة المنصورة الجديدة

PHYSICS LAB

Filters

رؤية
20/30
VISION OF EGYPT

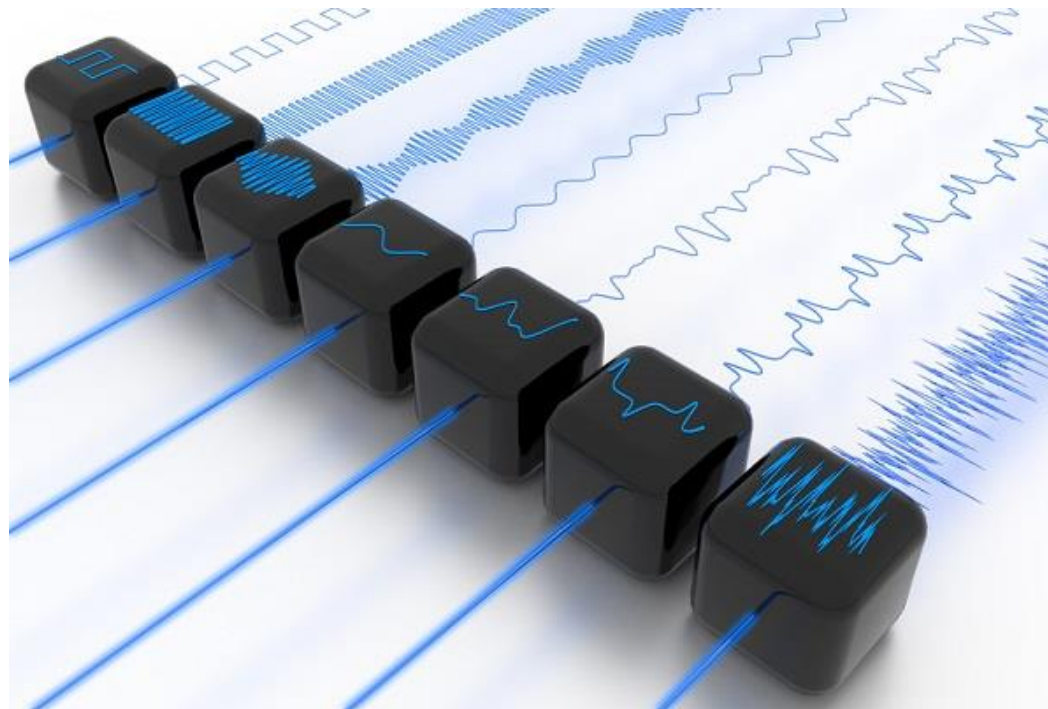RF filter solutions play an important role to improve the quality of the received signals by avoiding (filtering out) unnecessary frequency components from the received spectrum. This is significant at receiving end since the signal strength is often too low at the receivers. Any noise could potentially impact the received signal quality and thus information loss.



The most important types of filters are *Low pass filters* and *high pass filters*.

1- High pass filters

This type of filters prevents low frequency range and passes high frequencies.

Applications of Low pass filters

- HPFs are used to reject any low-frequency components for the system
- In audio devices HPFs are used to filter low-frequency components below 2.5 kHz.
- RF laboratories use HPFs to build various test setups which require low-frequency isolation.
- High Pass Filters are used in harmonics measurements to avoid fundamental signals from the source and only allow high-frequency harmonics range.
- HPFs are used in radio receivers and satellite technology to attenuate low-frequency noise.

2- Low pass filters

This type of filters prevents high frequency range and passes low frequencies.

Applications of Low pass filters

- *Cut off high-frequency components in any system above its operating frequency range.*
- *Low pass filters are used in radio receivers to avoid high-frequency interference. Example: FM radio broadcasting operates at 88MHz to 108 MHz range, a low pass filter with a cut-off frequency just above 108MHz is used in FM radio receivers.*
- *In audio devices, low pass filters are used to filter treble sound from 2.5 kHz to 20 kHz (high-frequency components of the audio spectrum) to subwoofers. This frequency selection significantly improves the audio quality. Each speaker (subwoofer, mid-range speakers, and tweeter) is designed to operate within a specific frequency range.*
- *In RF test laboratories, low pass filters are used to construct complex test setups. The main purpose of low pass filters is to avoid high-frequency interference and improve test setup accuracy.*

In AC Circuits


For capacitors



Capacitor: $X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$

• When f increase $\Rightarrow X_C$ decrease

For inductors

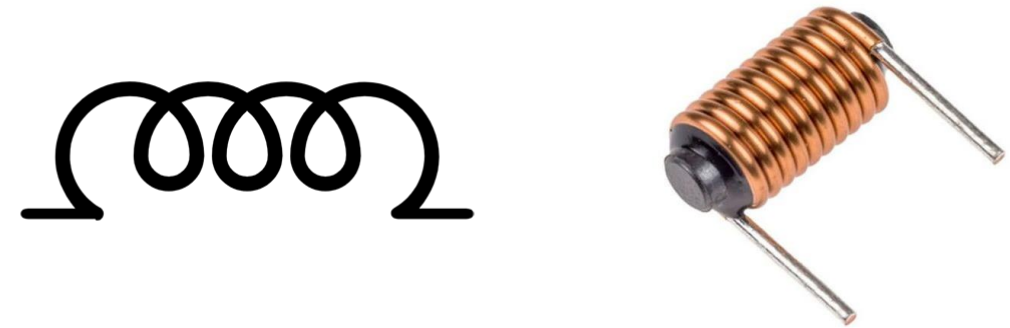

Inductor: $X_L = \omega L = 2\pi f L$

• When f increase $\Rightarrow X_L$ increase

- ✓ Recognize the meaning of electronic filters and their usages.
- ✓ Recognize the meaning of Gain.
- ✓ Calculation the cutoff frequency in **RC circuits** by connecting low and high pass filter circuit.
- ✓ Calculation of Attenuation factor.


- *Function Generator*•




- *Oscilloscope*•



- *Capacitor*•

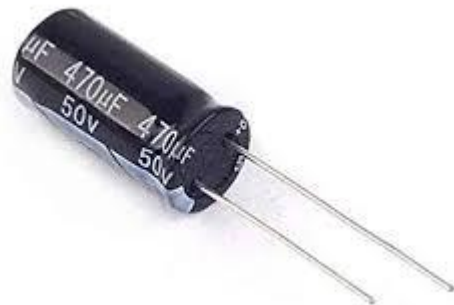

- *Bread board*•

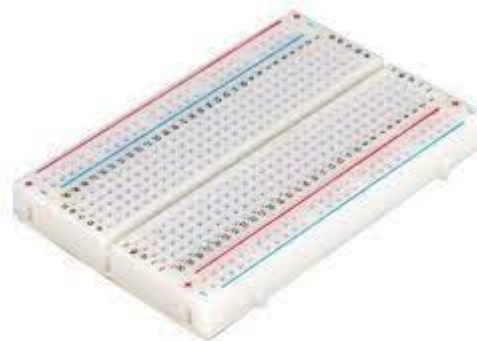

- *Resistor*•



High Pass filter using RC circuit.

$$V_{out} = \frac{R}{\sqrt{R^2 + (X_L - X_C)^2}} V_{in}$$


X_L here is not applicable i.e. equal zero

$$X_C = \frac{1}{2\pi fC}$$


So, if frequency f increases $\uparrow \Rightarrow X_C$ decreases \downarrow

V_{out} will increase \uparrow

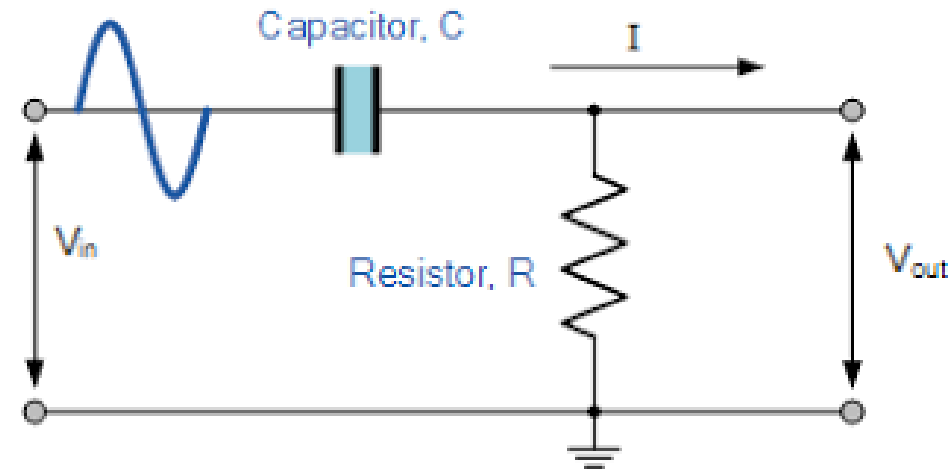Note that $\text{Gain(dB)} = 20 \log \left(\frac{V_{out}}{V_{in}} \right)$



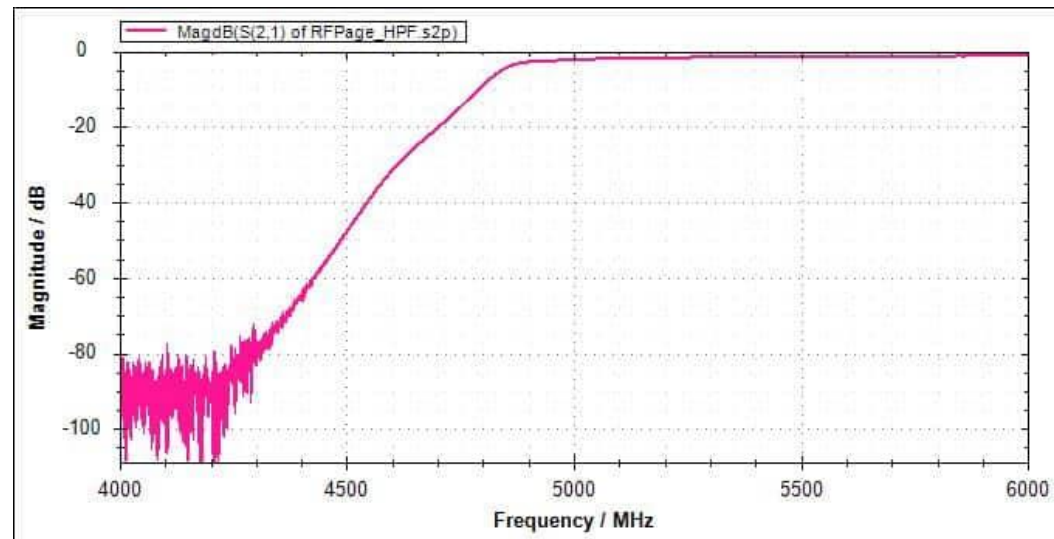Only High frequencies are allowed to pass



LOW Pass filter using RC circuit.

$$V_{out} = \frac{X_c}{\sqrt{R^2 + (X_L - X_C)^2}} V_{in}$$

X_L here is not applicable i.e. equal zero


$$X_C = \frac{1}{2\pi fC}$$

So, if frequency f increases $\uparrow \Rightarrow X_C$ decrease \uparrow


V_{out} will decrease \downarrow

Note that
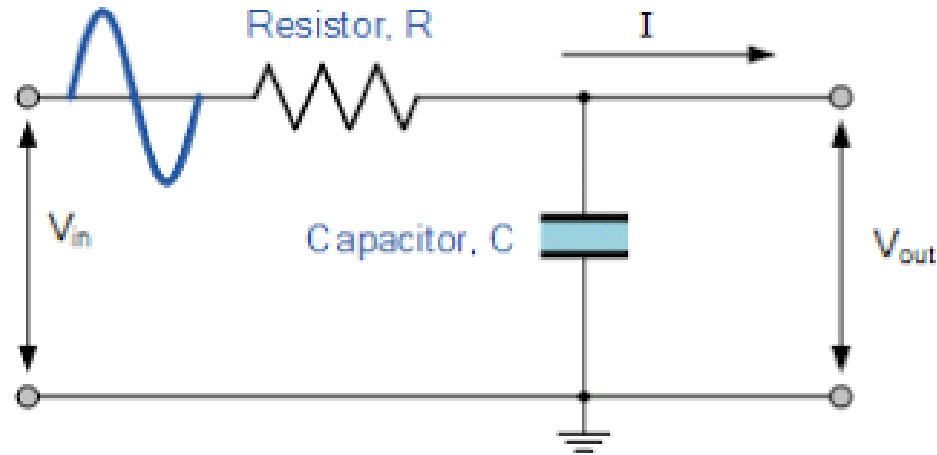
$$\text{Gain(dB)} = 20 \log \left(\frac{V_{out}}{V_{in}} \right)$$



Only low frequencies are allowed to pass

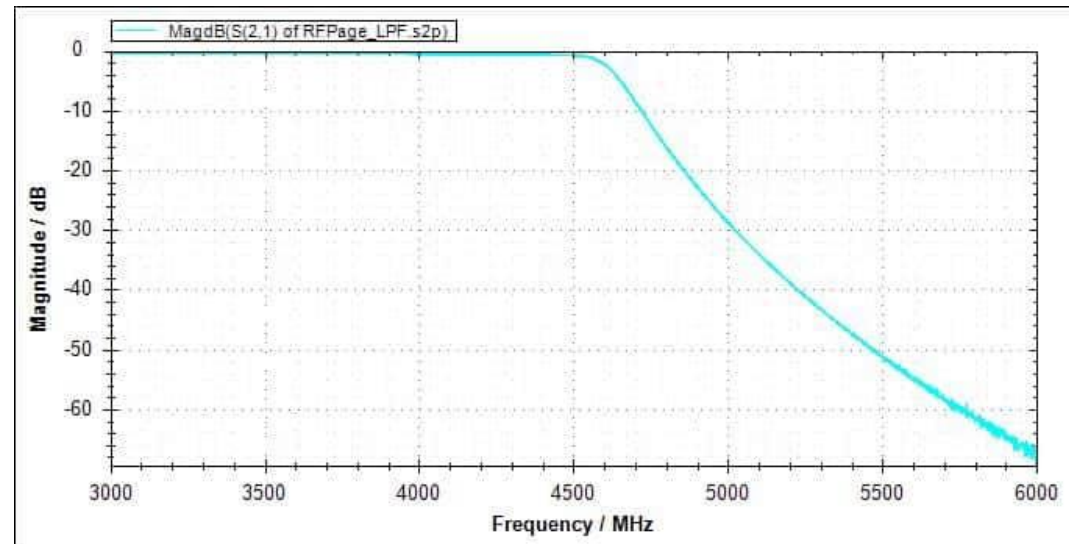

If two curves (High and low pass) are plotted together, the intercept of the two curves will denote the cutoff frequency.

At cutoff frequency.

$$V_R = V_C$$

$$I_R = I_C$$


$$R = \frac{1}{\omega_0 C} = \frac{1}{2 \pi f_c C}$$

$$f_c = \frac{1}{2 \pi R C}$$

Attenuation Factor: α

$$\alpha = 1 - G$$

$$= 1 - \frac{V_{out}}{V_{in}}$$

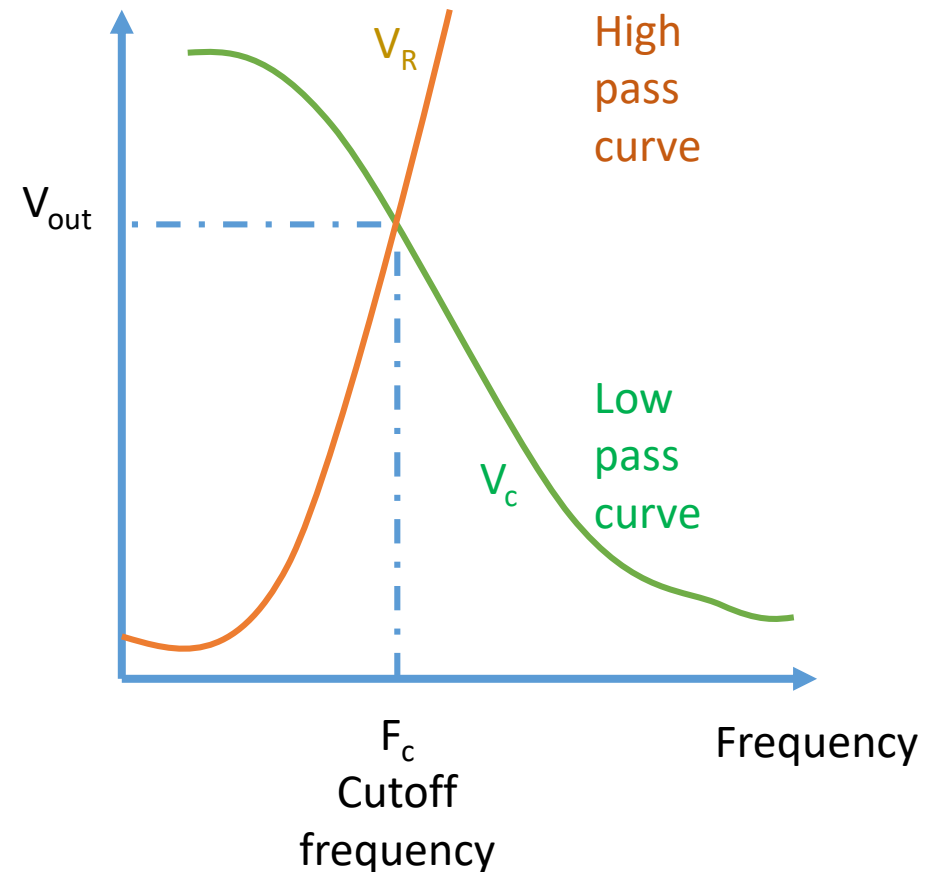

1. Connect the circuit as shown in Figure.
2. Vary the value of frequency f and determines V_{out} on the oscilloscope.
3. Connect the circuit as shown in Figure.
4. Vary the value of frequency f and determines V_{out} on the oscilloscope.

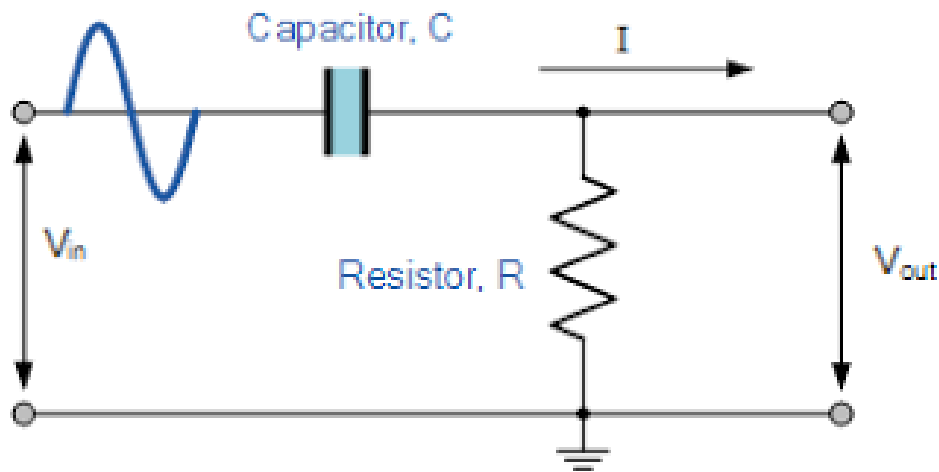


Fig. 1

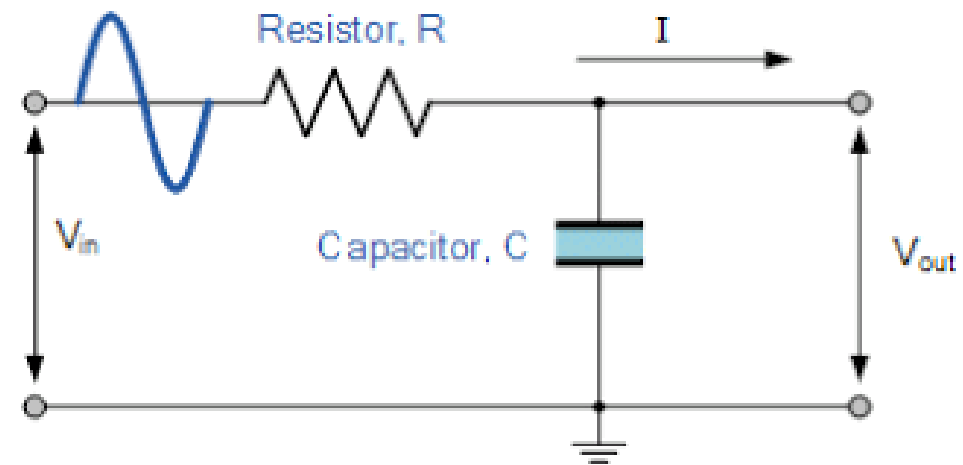


Fig. 2

High pass curve


F (Hz)						
V_{out}						

Low pass curve

F (Hz)						
V_{out}						

$$F_c = \dots\dots\dots$$

$$\alpha = \dots\dots\dots$$

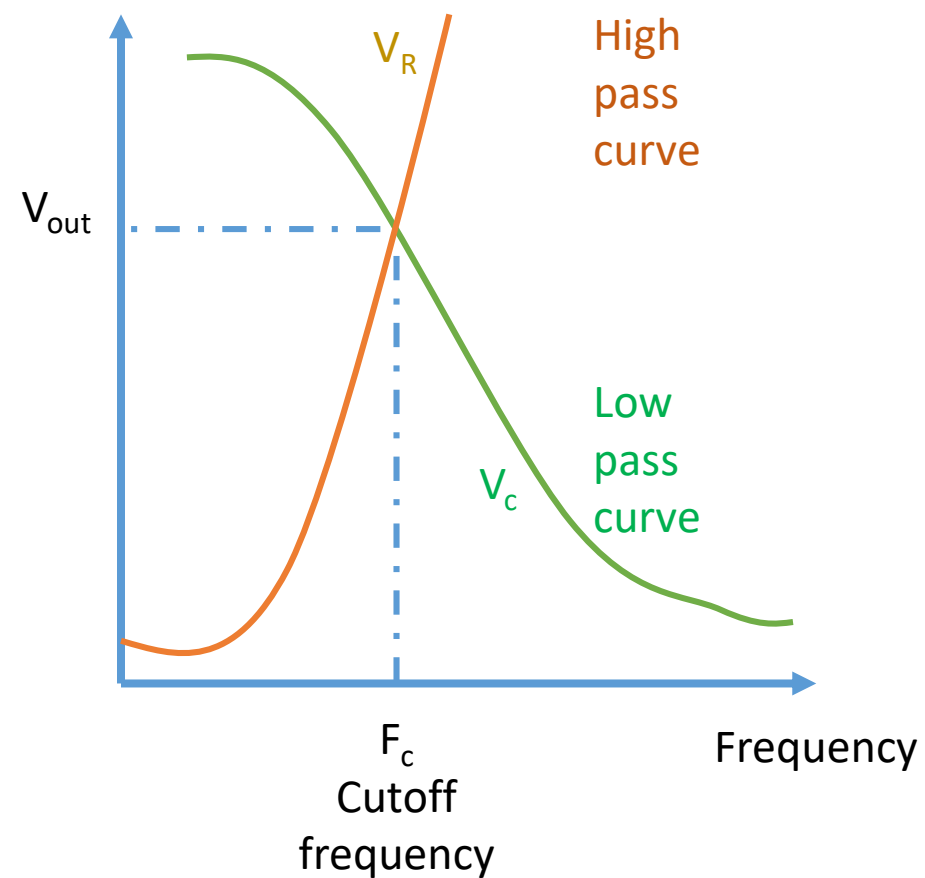



THANK YOU

