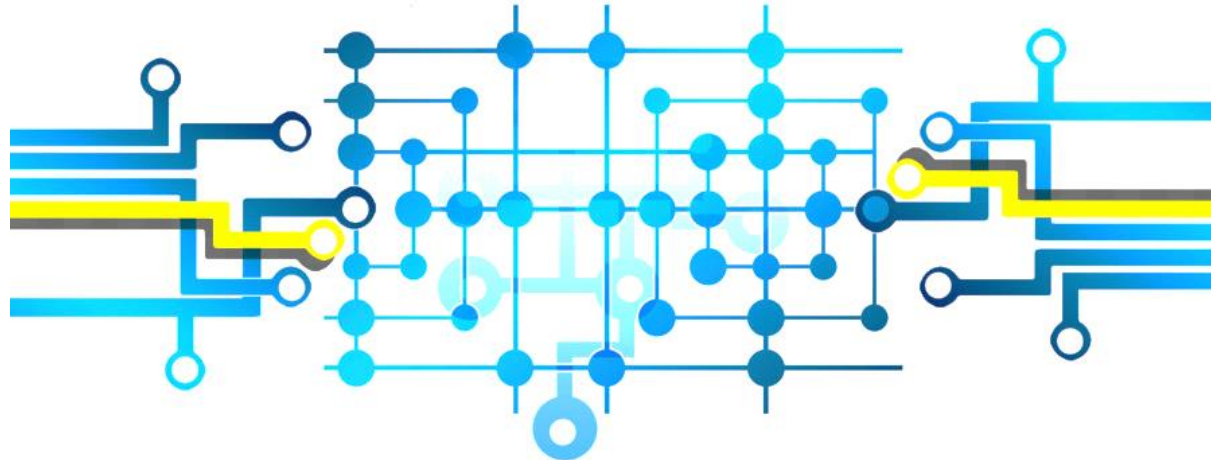


Circuit Analysis and Circuit Theorems

CSE 113




Physics Department
Faculty of Science
New Mansoura University

OUTLINES




- ❑ Independent Vs. Dependent Sources
- ❑ Kirchhoff's Laws
- ❑ Nodal Analysis
- ❑ Supernode
- ❑ Mesh Analysis
- ❑ Super-Mesh
- ❑ Circuit Theorems
 - Circuit linearity
 - Superposition
 - Source transformation
 - Thevenin's theorem
 - Norton theorem

Independent Vs. Dependent Sources

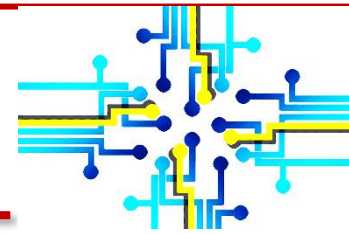


- Sources in which the voltage is completely independent of the current, or the current is completely independent of the voltage; these are termed **independent sources**.

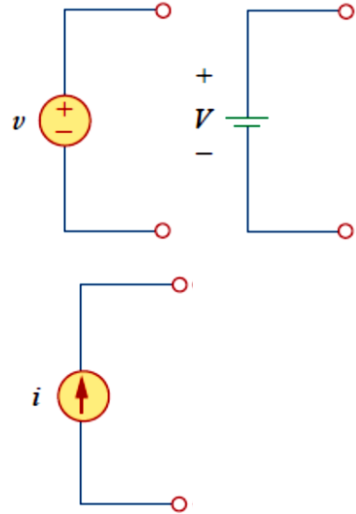- An independent voltage source is characterized by the terminal voltage which is completely independent of the current through it.
- For an independent current source, the current through the element is completely independent of the voltage across it.



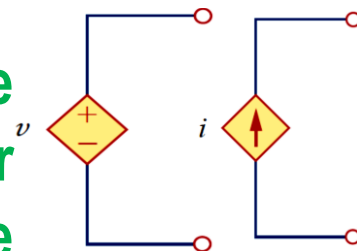
- Particular kinds of sources for which either the source voltage or current depends upon current or voltage elsewhere in the circuit; such sources are referred to as **dependent sources**.



Dependent Sources

- Dependent sources are useful in modelling elements such as transistors, operational amplifiers, and integrated circuits.
- Dependent sources are usually designated by diamond-shaped symbols.
- Voltage source comes with polarities (+ -) in its symbol, while a current source comes with a narrow, irrespective of what it depends on.
- The four different types of dependent sources:

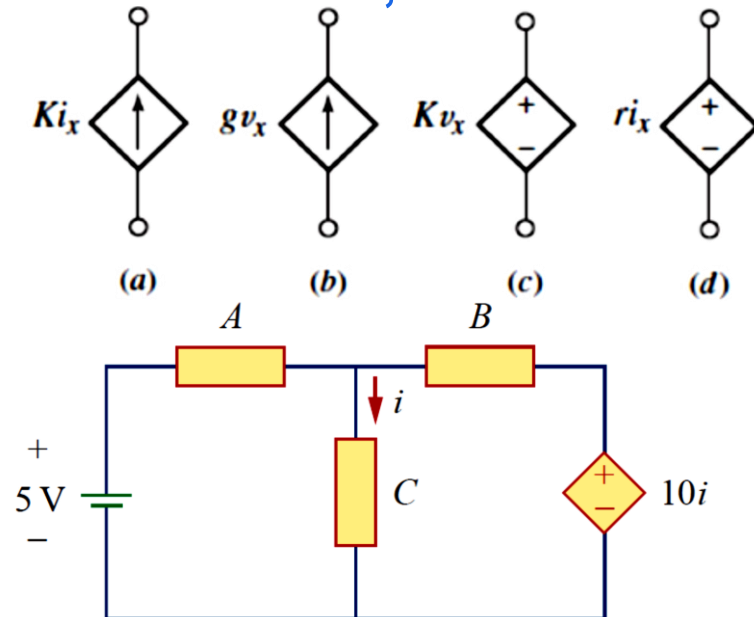
- (a) current-controlled current source;
- (b) voltage-controlled current source;
- (c) voltage-controlled voltage source;
- (d) current controlled voltage source.




Series and parallel connection of sources



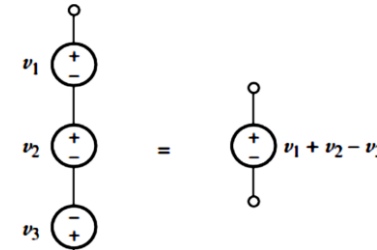
- Series-connected voltage sources can be replaced by a single source.



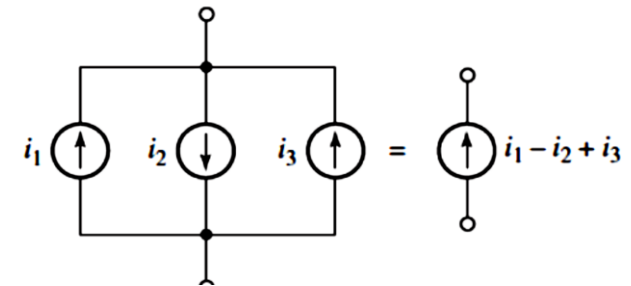
- Parallel current sources can be replaced by a single source.



- Voltage Sources in Parallel

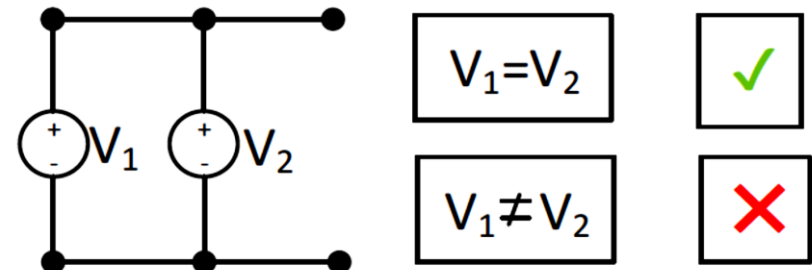

- Current Sources in Series

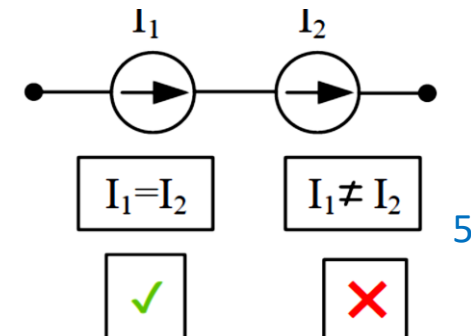

Kirchhoff's Laws



- ❑ Ohm's law is not sufficient for circuit analysis.
- ❑ Kirchhoff's laws complete the needed tools.

There are two laws:

- Current law.
- Voltage law.


Kirchhoff's current law (KCL)



- ❑ Kirchhoff's current law is based on conservation of charge.
- ❑ It states that the algebraic sum of currents entering a node (or a closed boundary) is zero.
- ❑ It can be expressed as:

$$\sum_{n=1}^N i_n = 0$$

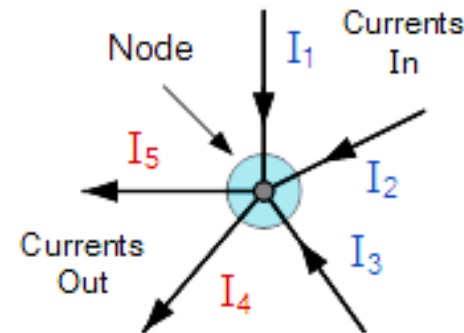Currents Entering the Node
Equals
Currents Leaving the Node




$$I_1 + I_2 + I_3 + (-I_4 + -I_5) = 0$$

Kirchhoff's voltage law (KVL)



- ❑ Kirchhoff's voltage law is based on conservation of energy.
- ❑ It states that the algebraic sum of currents around a closed path (or loop) is zero.
- ❑ It can be expressed as

$$\sum_{m=1}^M v_m = 0$$

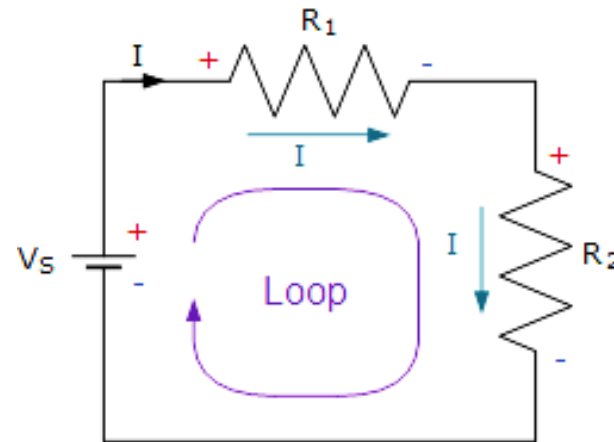


Nodal Analysis




□ Steps to Determine Node Voltages:

- Select a node as the reference node. Assign voltage V_1 , V_2 , ..., V_{n-1} to the remaining $n-1$ nodes. The voltages are referenced with respect to the reference node.
- Apply **KCL** to each of the $n-1$ nonreference nodes. Use Ohm's law to express the branch currents in terms of node voltages.
- Solve the resulting simultaneous equations to obtain the unknown node voltages.


Example 2

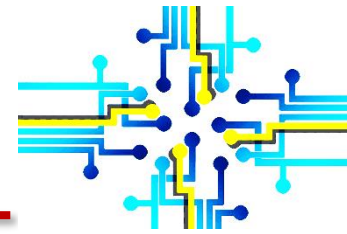

□ Typical circuit for nodal analysis

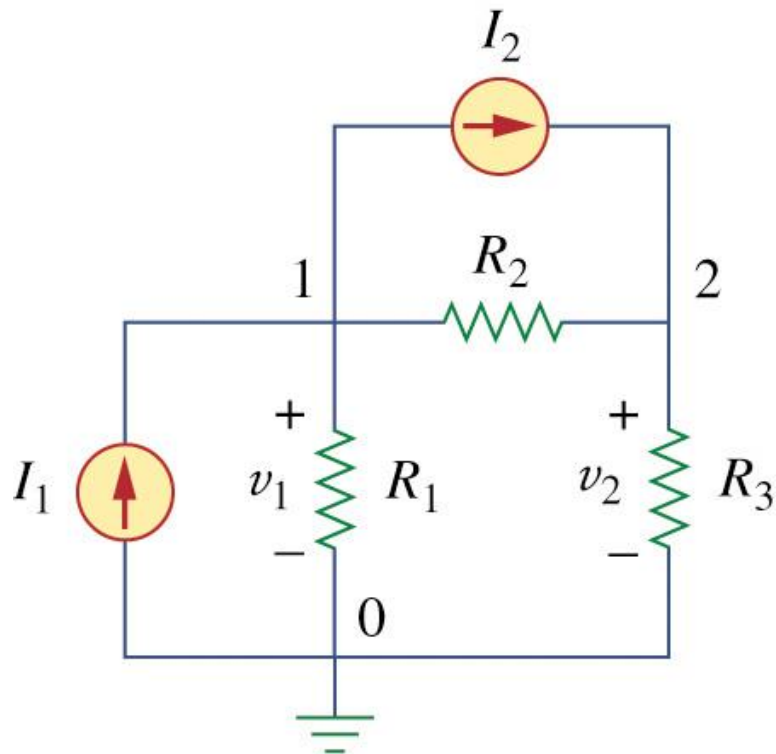

(a)

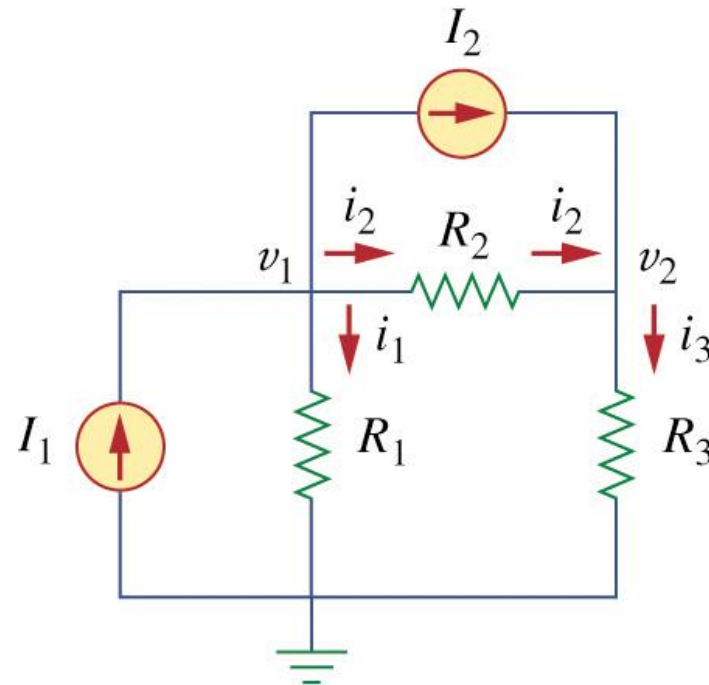

(b)

Example 2



$$I_1 = I_2 + i_1 + i_2$$


$$I_2 + i_2 = i_3$$

$$i = \frac{v_{\text{higher}} - v_{\text{lower}}}{R}$$

$$i_1 = \frac{v_1 - 0}{R_1} \quad \text{or} \quad i_1 = G_1 v_1$$

$$i_2 = \frac{v_1 - v_2}{R_2} \quad \text{or} \quad i_2 = G_2 (v_1 - v_2)$$

$$i_3 = \frac{v_2 - 0}{R_3} \quad \text{or} \quad i_3 = G_3 v_2$$

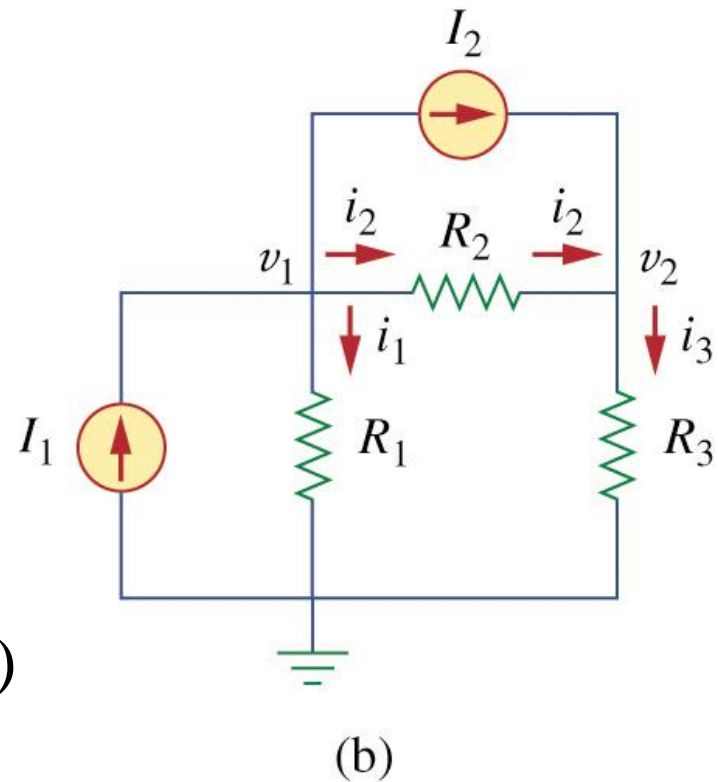

Example 2




$$\Rightarrow I_1 = I_2 + \frac{v_1}{R_1} + \frac{v_1 - v_2}{R_2}$$

$$I_2 + \frac{v_1 - v_2}{R_2} = \frac{v_2}{R_3}$$


$$\Rightarrow I_1 - I_2 = G_1 v_1 + G_2 (v_1 - v_2)$$

$$I_2 = -G_2 (v_1 - v_2) + G_3 v_2$$

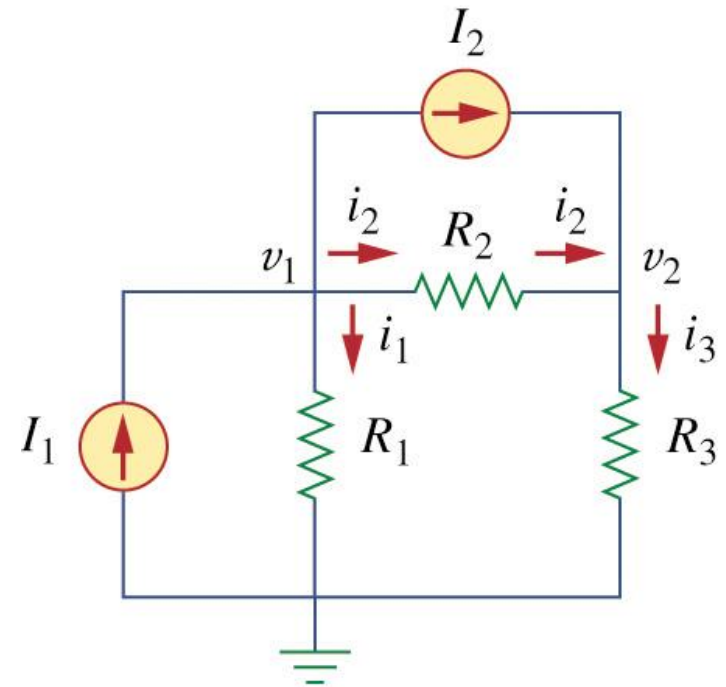


(b)


Nodal Analysis with Voltage Sources

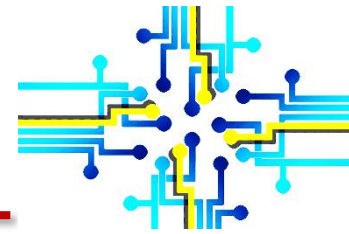

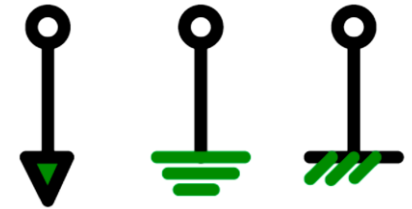- **Case 1:** The voltage source is connected between a nonreference node and the reference node: The nonreference node voltage is equal to the magnitude of voltage source and the number of unknown nonreference nodes is reduced by one.
- **Case 2:** The voltage source is connected between two nonreferenced nodes: a generalized node (supernode) is formed.



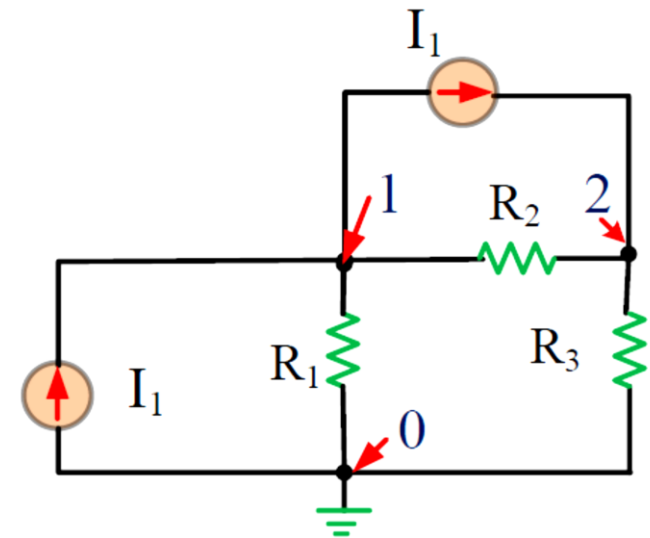
- **Node 0 is Reference node**
- **Nodes 1, 2 are Non-Reference node**



Supernode



- A **supernode** is formed by enclosing a (dependent or independent) voltage source connected between two nonreference nodes and any elements connected in parallel with it.
- The required two equations for regulating the two nonreference node voltages are obtained by the **KCL** of the **supernode** and the relationship of node voltages due to the voltage source.

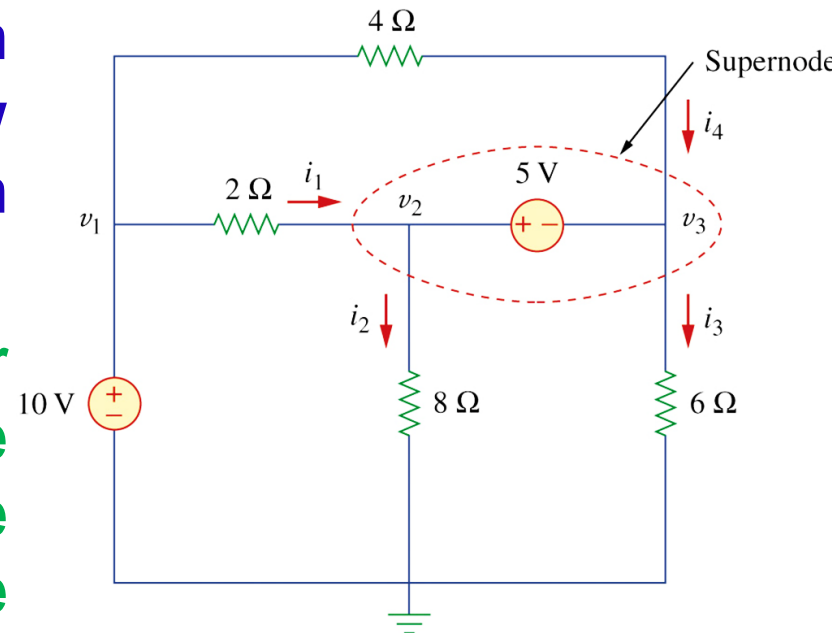

Example 1




□ For the circuit shown in Fig, find the node voltages.

$$2 - 7 - i_1 - i_2 = 0$$

$$2 - 7 - \frac{v_1}{2} - \frac{v_2}{4} = 0$$

$$v_1 - v_2 = -2$$

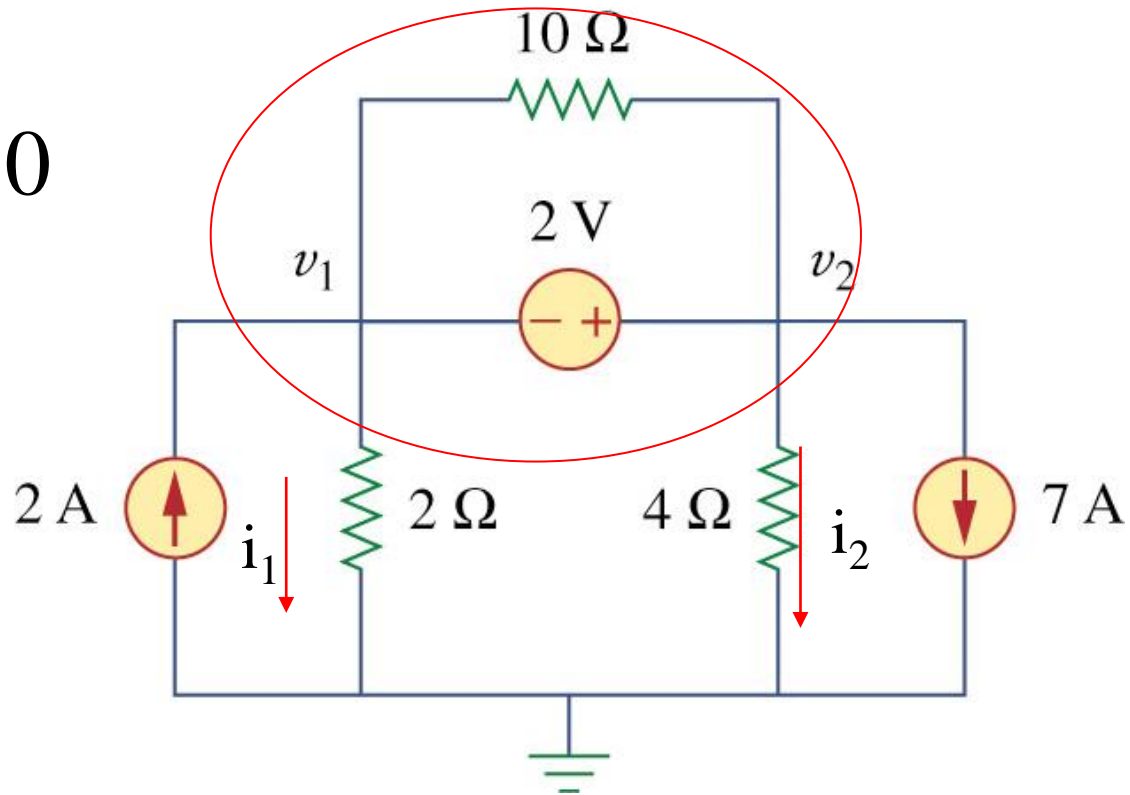

Mesh Analysis




- ❑ **Mesh analysis** helps us to solve complex electrical networks
- ❑ **Loop:** It is a closed path with no node passed more than once.
- ❑ **Mesh:** A mesh is a loop that does not contain any other loop within it.
- ❑ **Mesh analysis** is only applicable to a circuit that is **planar**.
- ❑ **Planar Circuit:** A planar circuit is one that can be drawn in a plane with no branches crossing one another.
- ❑ **Non-Planar Circuit:** A nonplanar circuit is one that can be drawn in a plane with branches crossing one another.


Mesh Analysis



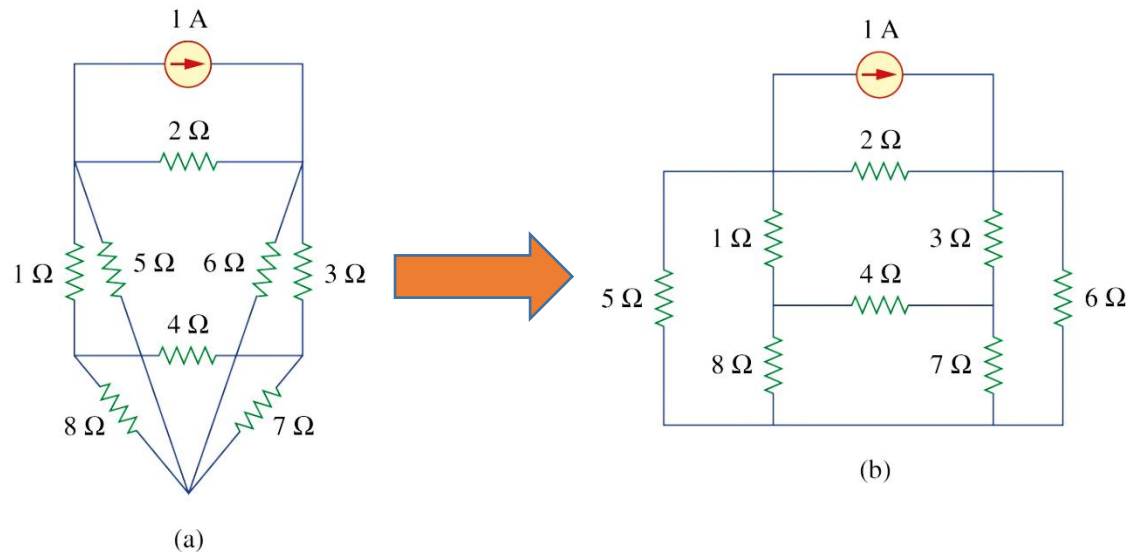
- A Planar circuit with crossing branches,
- The same circuit redrawn with no crossing branches.



- A nonplanar circuit.

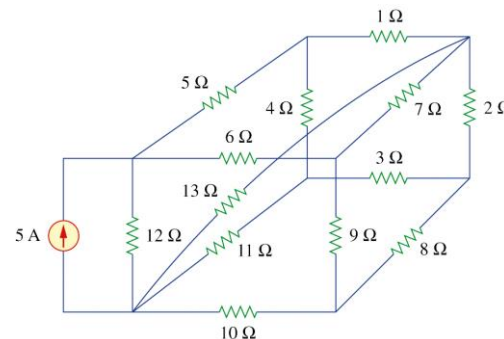

Mesh Analysis

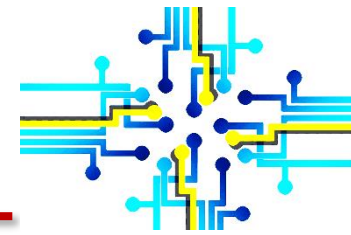

□ Steps to Determine Mesh Currents:

- Assign mesh currents i_1, i_2, \dots, i_n to the n meshes.
- Apply KVL to each of the n meshes. Use Ohm's law to express the voltages in terms of the mesh currents.
- Solve the resulting n simultaneous equations to get the mesh currents.

▪ A circuit with two meshes.

- Apply KVL to each mesh. For mesh 1,


$$-V_1 + R_1 i_1 + R_3 (i_1 - i_2) = 0$$

$$(R_1 + R_3) i_1 - R_3 i_2 = V_1$$

- For mesh 2,

$$R_2 i_2 + V_2 + R_3 (i_2 - i_1) = 0$$

$$-R_3 i_1 + (R_2 + R_3) i_2 = -V_2$$

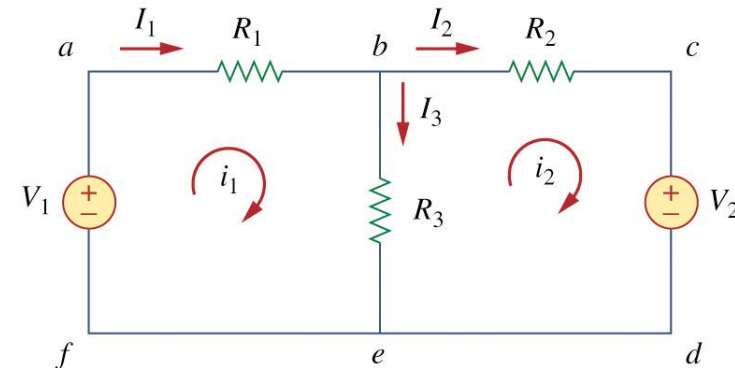


Mesh Analysis with Current Sources




□ Two cases arise in these circuits,


□ Current source exist in arm of a mesh

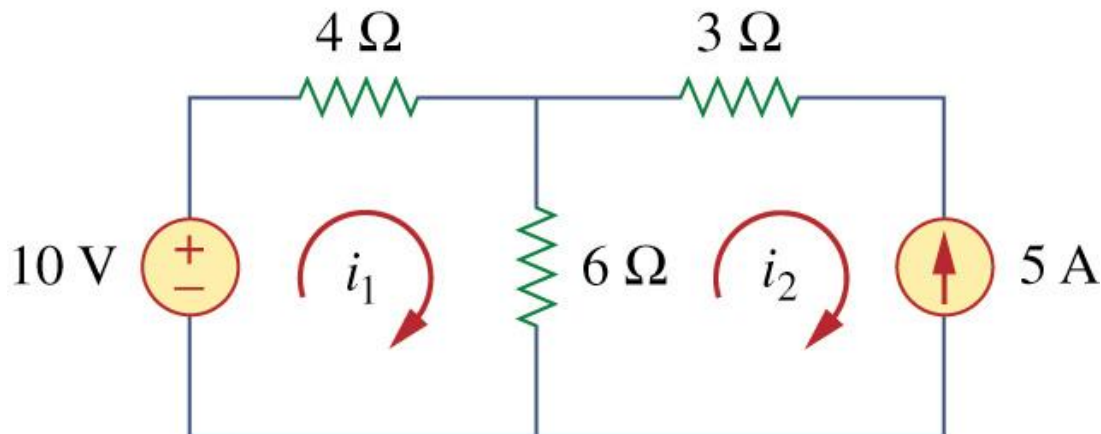

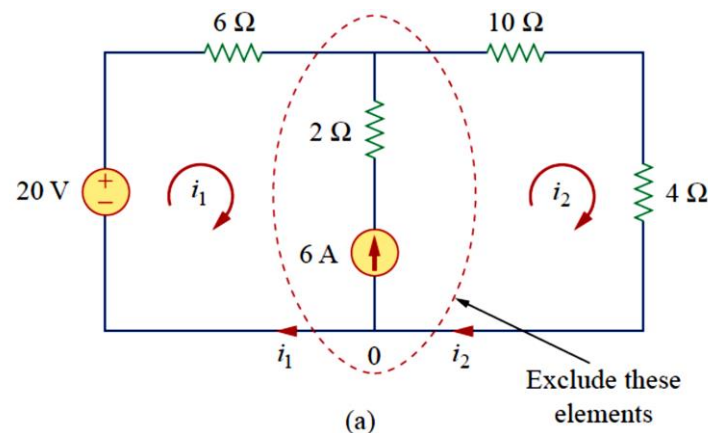
□ Current source exist in between meshes.




Super Mesh Concept

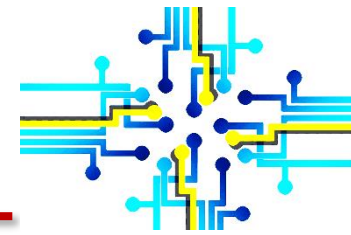

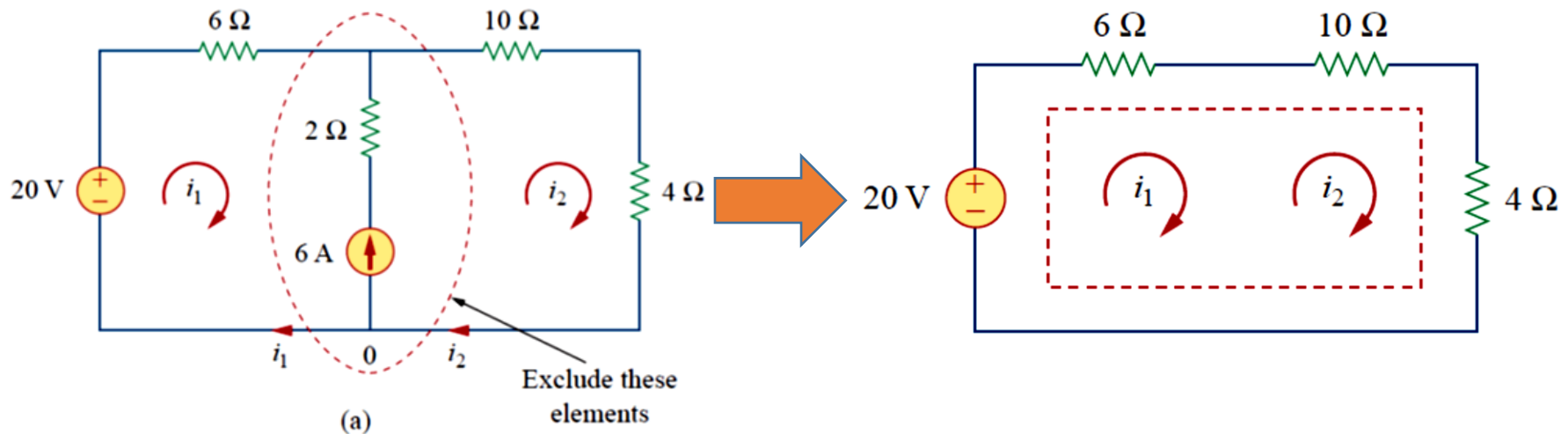- a super-mesh results when two meshes have a (dependent, independent) current source in common.
- We create a **super-mesh** by excluding the current source and any elements connected in series with it while taking **KVL**.



Super Mesh Concept

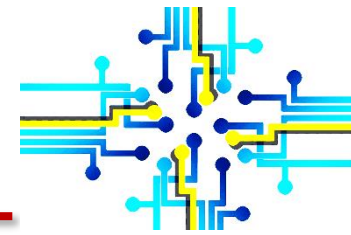

- Applying KVL to the super-mesh.


$$6i_1 + 10i_2 + 4i_2 = 20$$

$$6i_1 + 14i_2 = 20$$

- applying KCL at bottom node,

$$i_1 - i_2 = -6$$

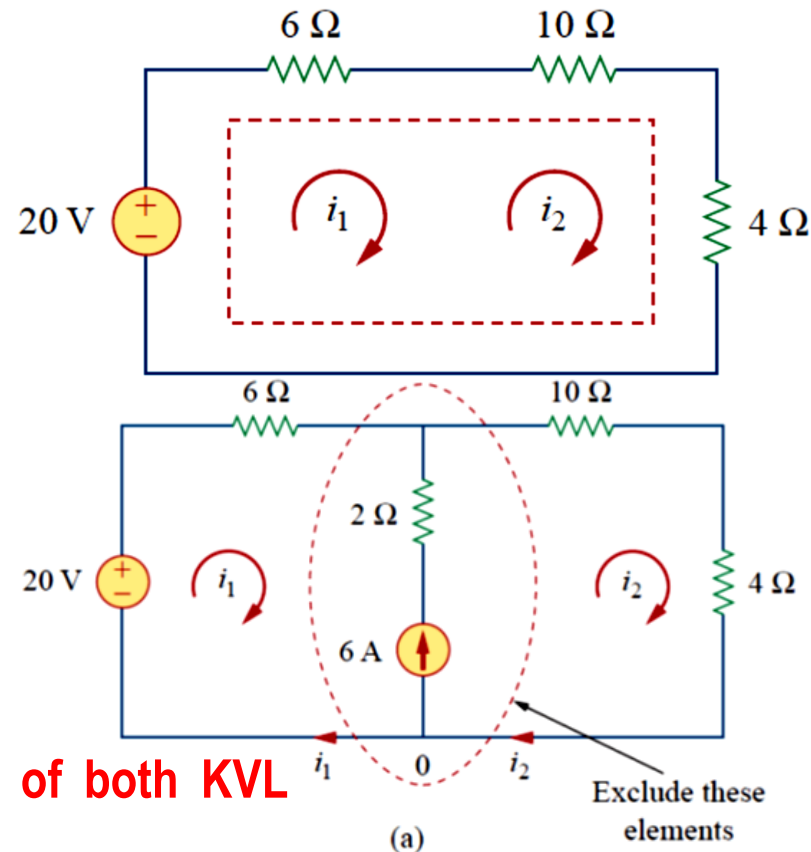- A super-mesh requires the application of both KVL and KCL.
- Similarly, a super-mesh formed from three meshes needs three equations: one is from the super-mesh and the other two equations are obtained from the two current sources.



NODAL ANALYSIS VS MESH ANALYSIS




Nodal Analysis

- ❑ The number of voltage variables, and hence simultaneous equations to solve, equals the number of nodes minus one.
- ❑ Every voltage source connected to the reference node reduces the number of unknowns by one.
- ❑ Nodal analysis is thus best for circuits with voltage sources.

Mesh analysis


- ❑ The number of current variables, and hence simultaneous equations to solve, equals the number of meshes.
- ❑ Every current source in a mesh reduces the number of unknowns by one.
- ❑ Mesh analysis is thus best for circuits with current sources.

Circuit Theorems

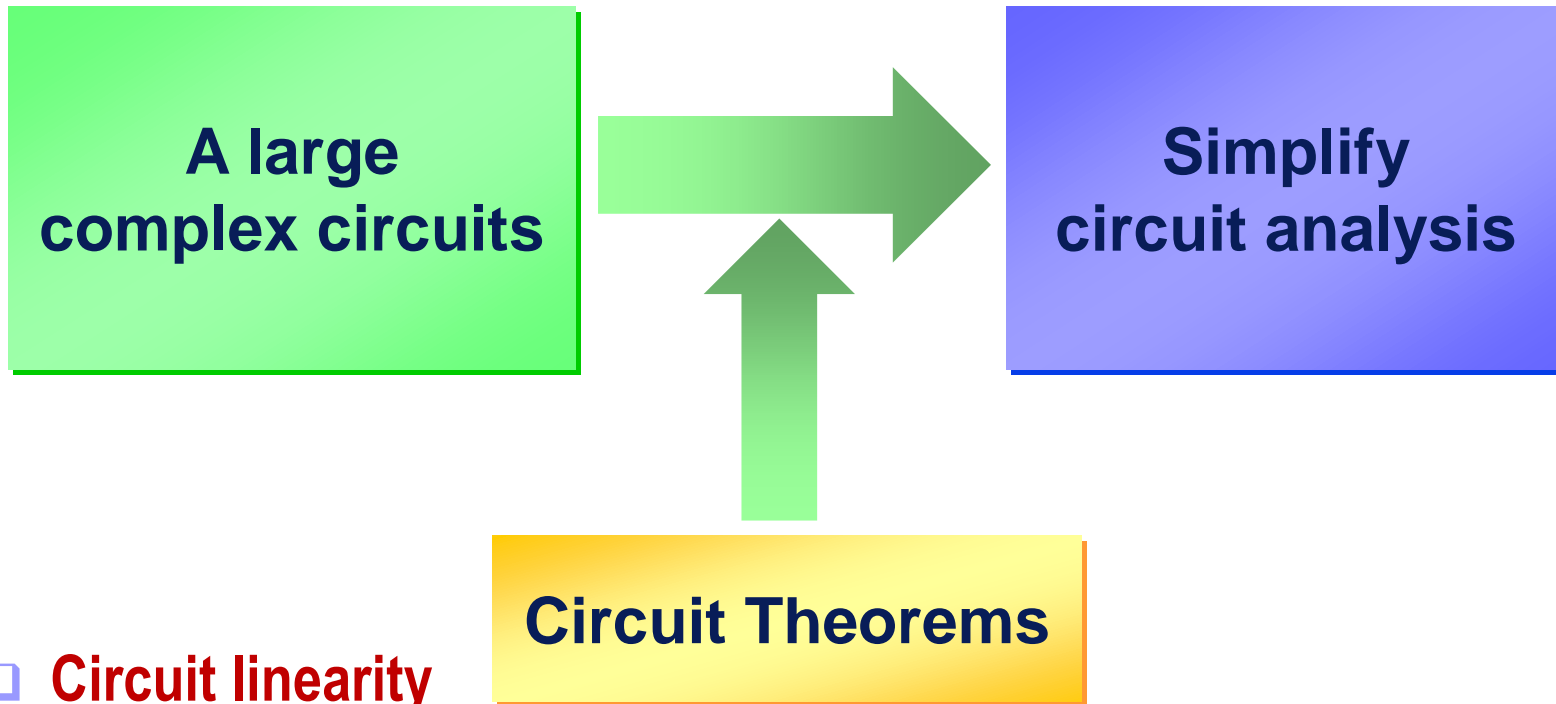

- ☐ **Circuit linearity**
- ☐ **Superposition**
- ☐ **Source transformation**
- ☐ **Thevenin's theorem**
- ☐ **Norton theorem**

Linearity Property

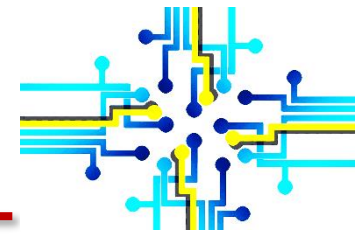


The property is a combination of both the homogeneity (scaling) property and the additivity property.

- The homogeneity property requires that if the input (also called the excitation) is multiplied by a constant, then the output (also called the response) is multiplied by the same constant.

$$V = I R \rightarrow KV = KI R$$

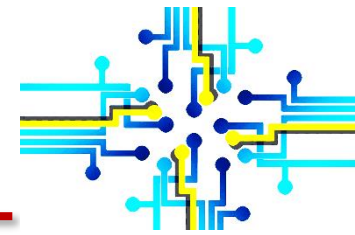- A linear circuit is one whose output is linearly related (or directly proportional) to its input.



Linearity Property

- The additivity property requires that the response to a sum of inputs is the sum of the responses to each input applied separately.


$$v_1 = i_1 R \quad \text{and} \quad v_2 = i_2 R$$

then applying $(i_1 + i_2)$ gives


$$v = (i_1 + i_2)R = i_1 R + i_2 R = v_1 + v_2$$

- We say that a resistor is a linear element because the voltage-current relationship satisfies both the homogeneity and the additivity properties.

Linearity Property

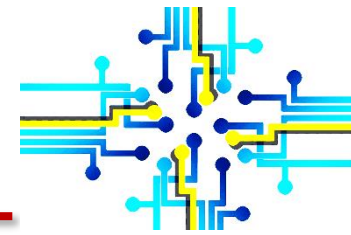

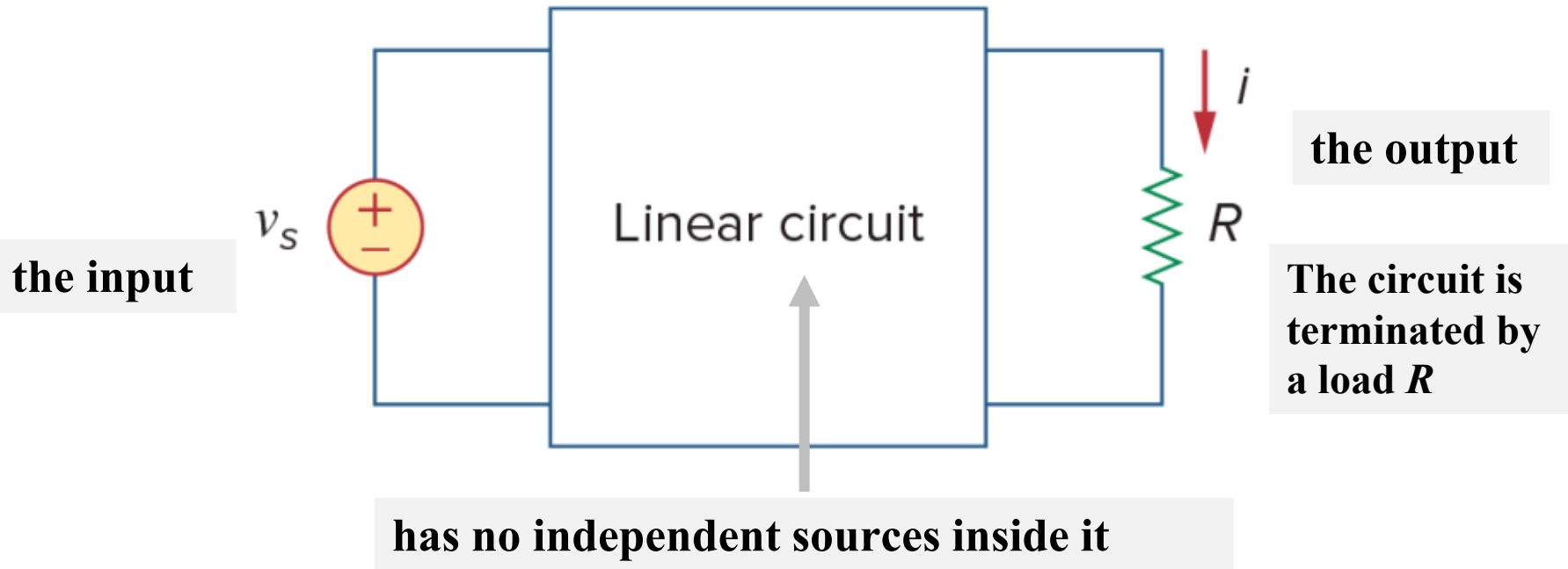- A linear circuit is one whose output is linearly related (or directly proportional) to its input



- Example

$$v_s = 10V \rightarrow i = 2A$$

$$v_s = 1V \rightarrow i = 0.2A$$

$$v_s = 5mV \leftarrow i = 1mA$$

$$p = i^2 R = \frac{v^2}{R} : \text{nonlinear}$$

Example 3



□ For the circuit in fig, find I_0 when $v_s=12V$ and $v_s=24V$.

□ KVL

$$12i_1 - 4i_2 + v_s = 0 \quad (1.1)$$


$$-4i_1 + 16i_2 - 3v_x - v_s = 0 \quad (1.2)$$


$$\text{But } v_x = 2i_1$$

$$\therefore -10i_1 + 16i_2 - v_s = 0 \quad (1.3)$$

From eqs(1.1) and (1.3) we get

$$2i_1 + 12i_2 = 0 \rightarrow i_1 = -6i_2$$

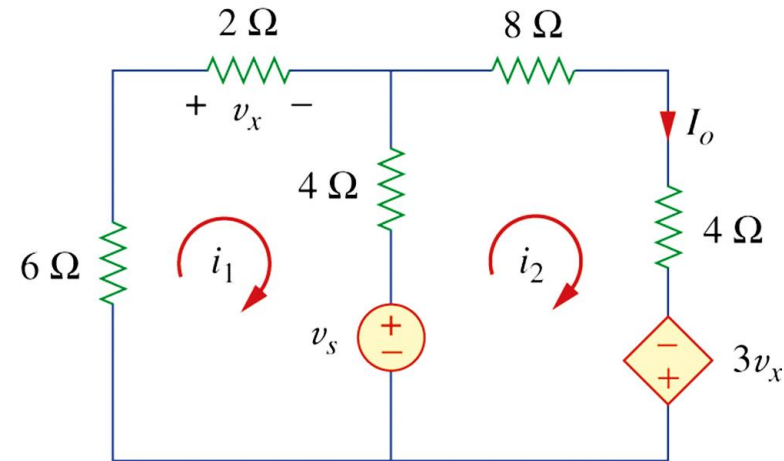

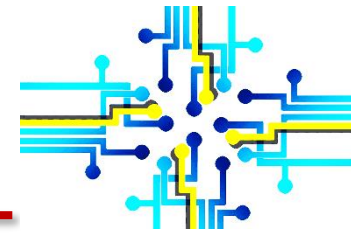

Example 3

Eq(1.1), we get

$$-76i_2 = v_s = 0 \Rightarrow i_2 = \frac{v_s}{76}$$

When

$$v_s = 12\text{V}$$

$$I_0 = i_2 = \frac{12}{76}\text{A}$$

When

$$v_s = 24\text{V}$$

$$I_0 = i_2 = \frac{24}{76}\text{A}$$

- Showing that when the source value is doubled, I_0 doubles.

Superposition



- ❑ The **superposition principle** states that the **voltage across (or current through)** an element in a linear circuit is the **algebraic sum** of the **voltages across (or currents through)** that element due to each **independent source acting alone**.
- ❑ **Turn off, killed, inactive source:**
 - independent voltage source: 0 V (short circuit)
 - independent current source: 0 A (open circuit)
- ❑ **Dependent sources are left intact because they are controlled by circuit variables.**

Superposition




□ Steps to apply superposition principle:

1. Turn off all independent sources except one source. Find the output (voltage or current) due to that active source using nodal or mesh analysis.
2. Repeat step 1 for each of the other independent sources.
3. Find the total contribution by adding algebraically all the contributions due to the independent sources.


□ How to turn off independent sources

- Turn off voltage sources = short voltage sources; make it equal to zero voltage
- Turn off current sources = open current sources; make it equal to zero current


Example 4

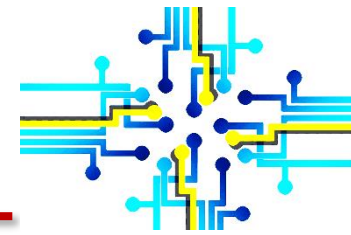

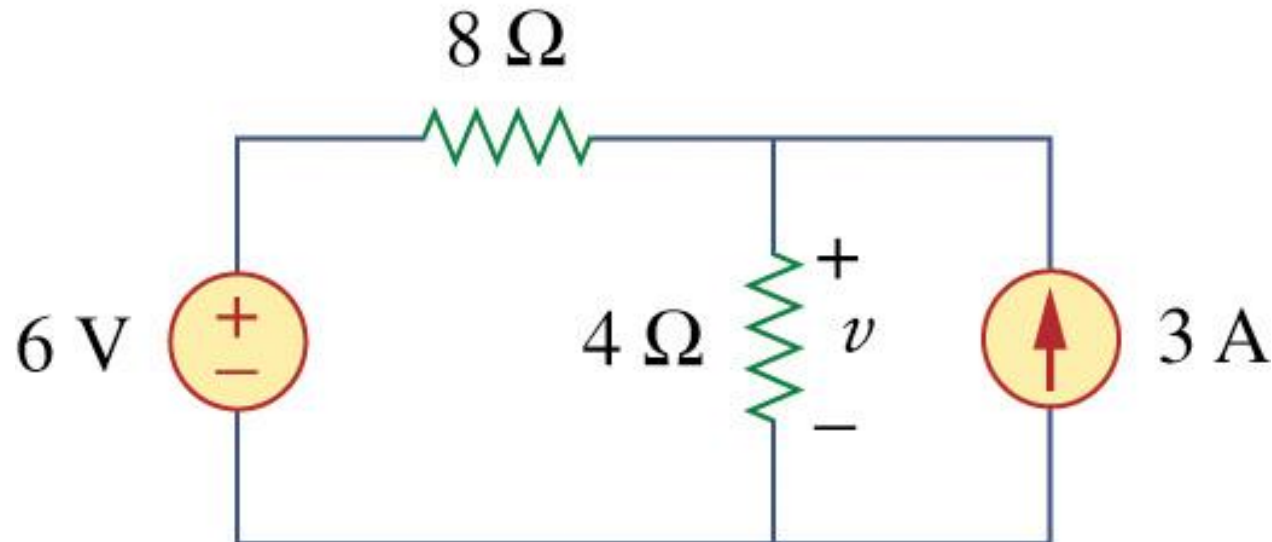Use the superposition theorem to find v in the circuit in Fig.




Voltage Division

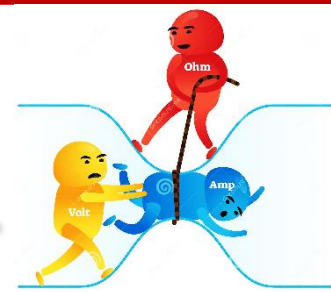


- The voltage drop across any one resistor can be known.
- The current through all the resistors is the same, so using Ohm's law:

$$v_1 = \frac{R_1}{R_1 + R_2} v \quad v_2 = \frac{R_2}{R_1 + R_2} v$$

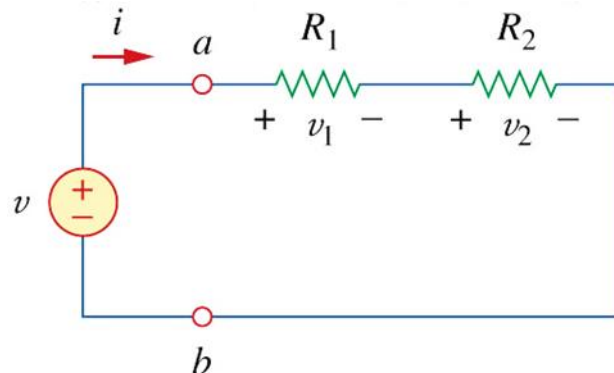- This is the principle of voltage division.



Current Division

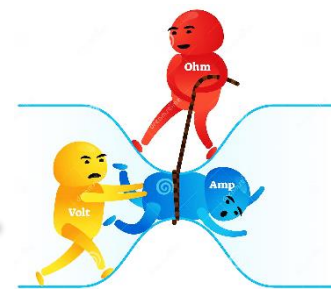


- Given the current entering the node, the voltage drop across the equivalent resistance will be the same as that for the individual resistors.


$$v = iR_{eq} = \frac{iR_1R_2}{R_1 + R_2}$$

- This can be used in combination with Ohm's law to get the current through each resistor:

$$i_1 = \frac{iR_2}{R_1 + R_2} \quad i_2 = \frac{iR_1}{R_1 + R_2}$$

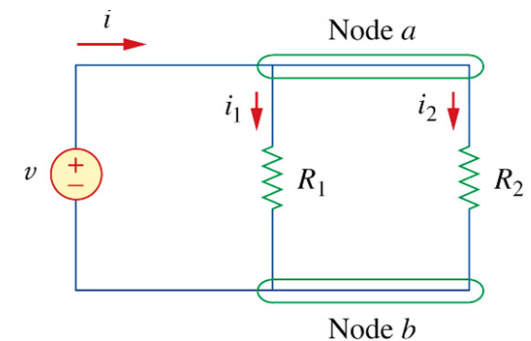

Example 4

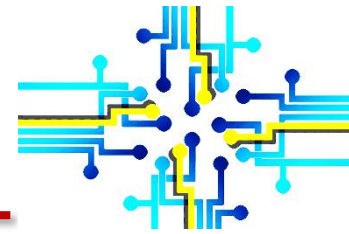

- Since there are two sources,
 - let $v = v_1 + v_2$
 - set the current source to zero
- Applying KVL to the loop

$$12i_1 - 6 = 0 \Rightarrow i_1 = 0.5 \text{ A}$$

$$v_1 = 4i_1 = 2 \text{ V}$$

- set the voltage source to zero
- Current division, to get


$$i_3 = \frac{8}{4+8}(3) = 2 \text{ A}$$

- Hence


$$v_2 = 4i_3 = 8 \text{ V}$$

- And we find


$$v = v_1 + v_2 = 2 + 8 = 10 \text{ V}$$

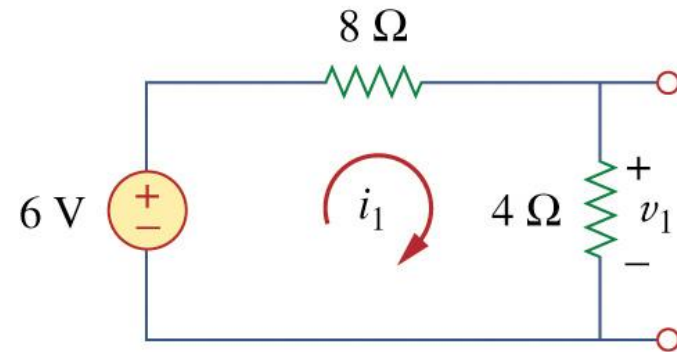

(a)

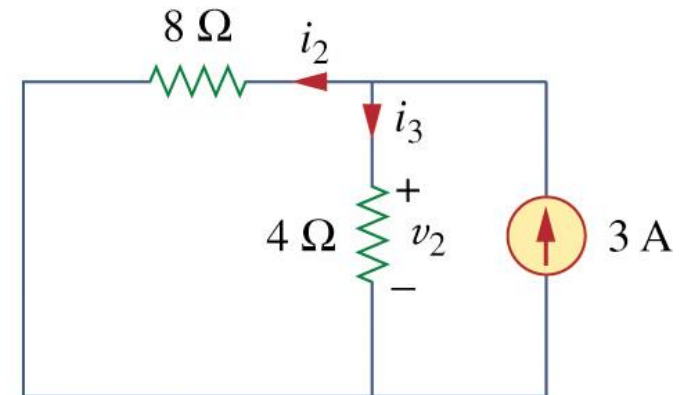


(b)

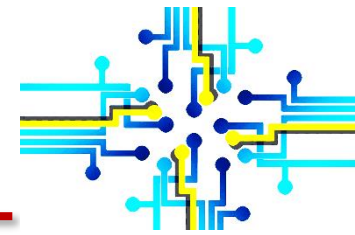



Source Transformation

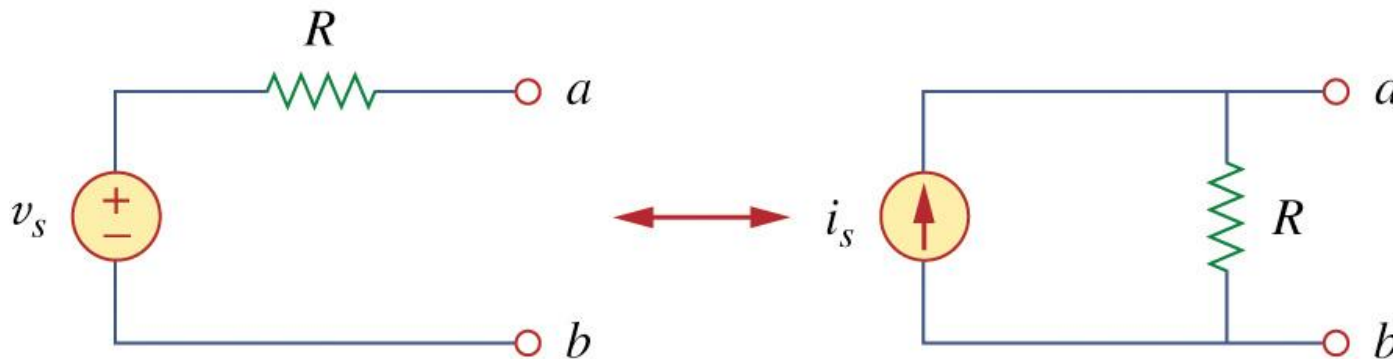- A source transformation is the process of replacing a voltage source v_s in series with a resistor R by a current source i_s in parallel with a resistor R , or vice versa
- a source transformation does not affect the remaining part of the circuit. When applicable, source transformation is a powerful tool that allows circuit manipulations to ease circuit analysis.



$$v_s = i_s R \quad \text{or} \quad i_s = \frac{v_s}{R}$$


Equivalent Circuits

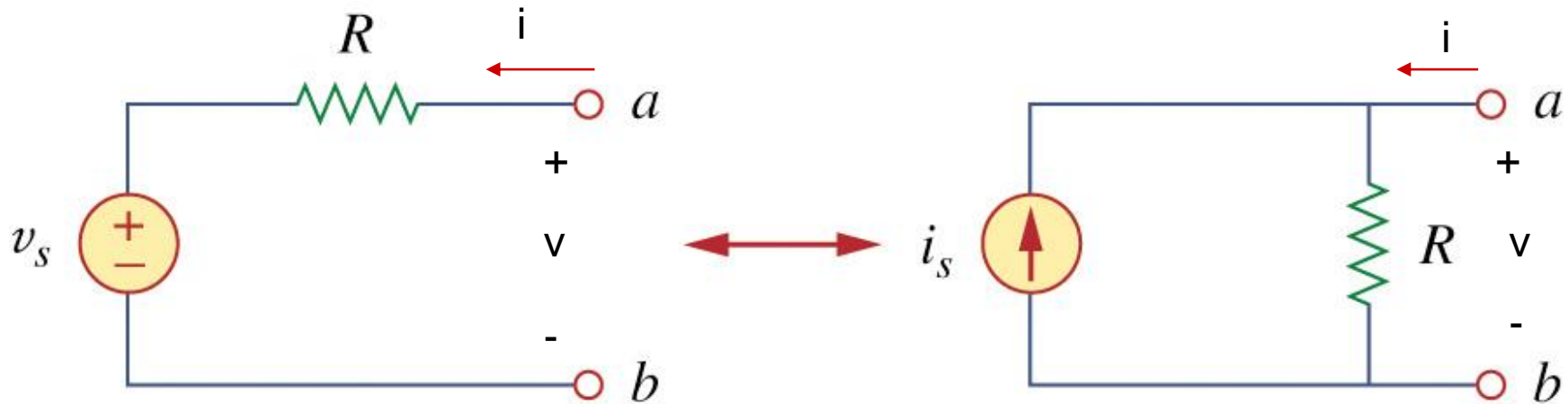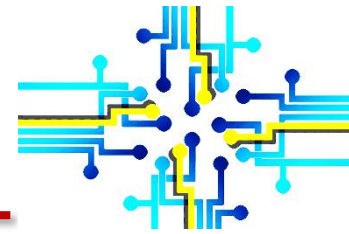


□ Arrow of the current source  positive terminal of voltage source


□ Impossible source Transformation

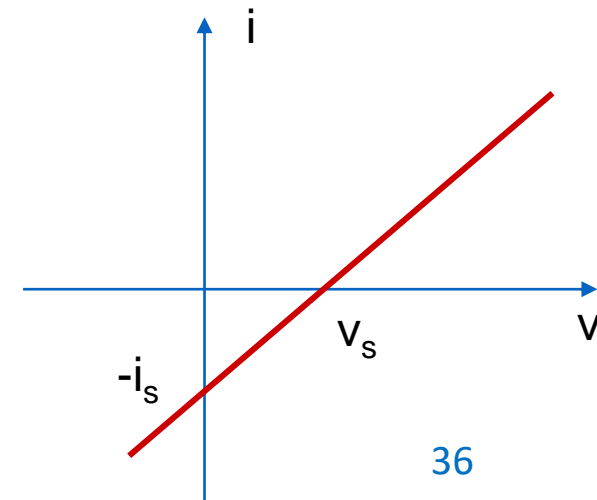- ideal voltage source ($R = 0$)
- ideal current source ($R = \infty$)



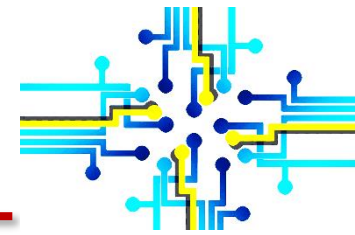


Source transformation rules

- ❑ Arrow of the current source  positive terminal of voltage source
- ❑ Impossible source Transformation
 - ideal voltage source ($R = 0$)
 - ideal current source ($R = \infty$)

Dependent Sources


- ❑ Source transformation also applies to dependent sources.
- ❑ But, the dependent variable must be handled carefully.
- ❑ The same relationship between the voltage and current holds here:

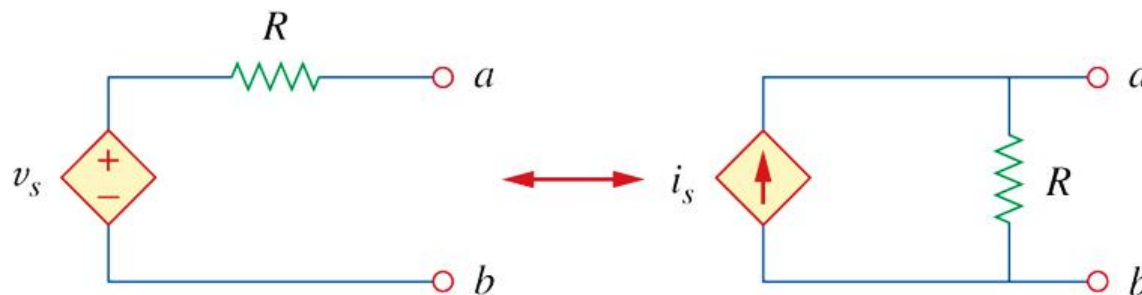

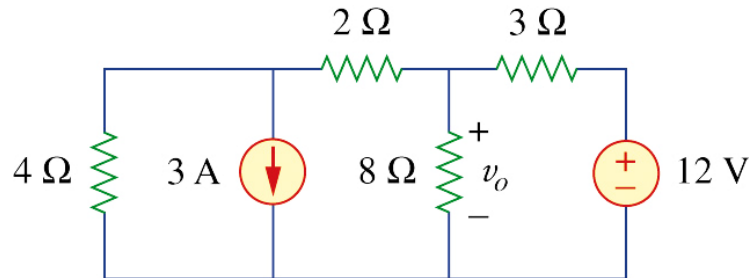
Example 5




Use source transformation to find v_o in the circuit in Fig



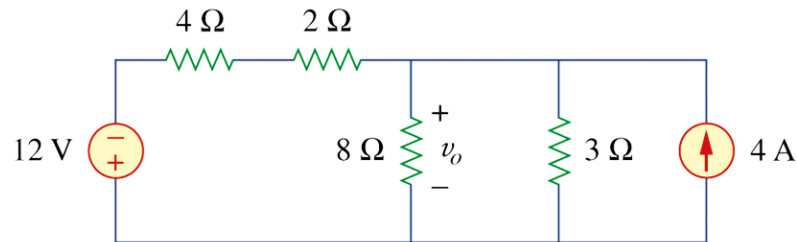- We first transform the current and voltage sources to obtain




- Combining the 2Ω and 6Ω resistors in series and transforming the 12-V voltage source gives

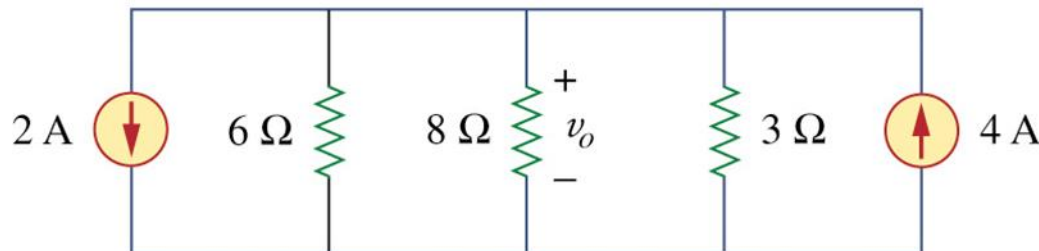

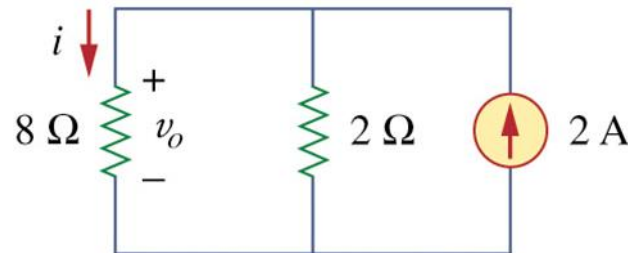Example 5



- We now combine the 6Ω and 3Ω resistors in parallel to get 2Ω . We also
- combine the 2-A and 4-A current sources to get a 2-A source



- we use current division in above Fig. to get


$$i = \frac{2}{2 + 8}(2) = 0.4\text{A}$$

$$v_o = 8i = 8(0.4) = 3.2\text{V}$$

Thevenin's Theorem




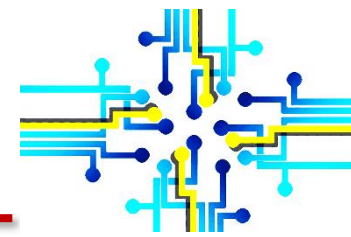- ❑ In many circuits, one element will be variable.
- ❑ An example of this is mains power; many different appliances may be plugged into the outlet, each presenting a different resistance.
- ❑ This variable element is called the load.
- ❑ Ordinarily one would have to reanalyze the circuit for each change in the load.




Thevenin's Theorem II

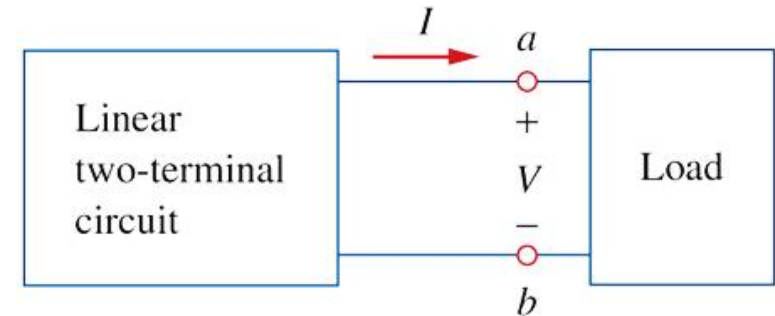- **Thevenin's theorem** states that a linear two terminal circuit may be replaced with a voltage source and resistor.
- The **voltage source's** V_{Th} value is equal to the open circuit voltage at the terminals.
- The **resistance** R_{Th} is equal to the resistance measured at the terminals when the independent sources are turned off.



(a)

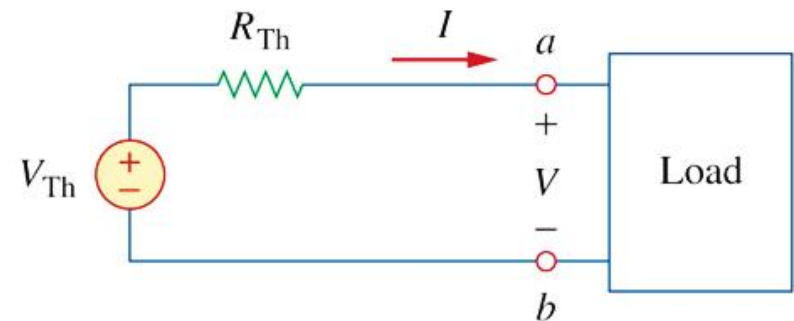


(b)

How to Find Thevenin's Voltage




- Equivalent circuit: same voltage-current relation at the terminals.

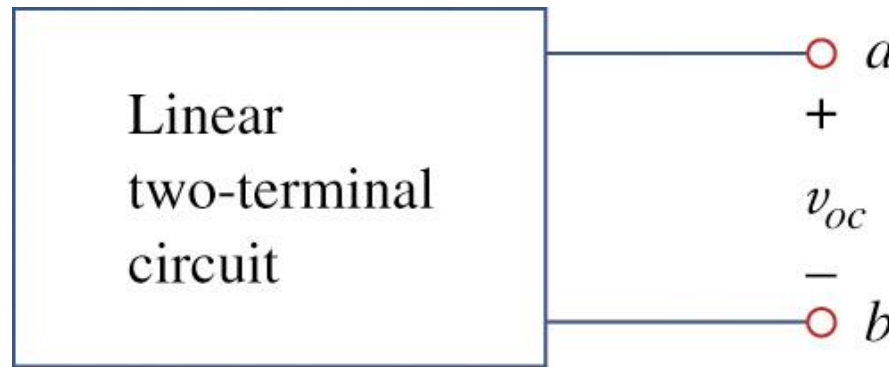$V_{Th} = v_{oc}$: open circuit voltage at $a - b$



$$V_{Th} = v_{oc}$$


How to Find Thevenin's Resistance

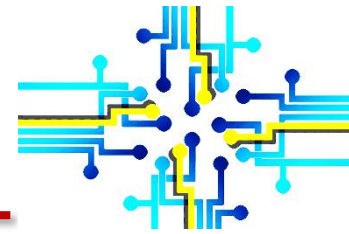

$$R_{Th} = R_{in} :$$

input – resistance of the dead circuit at $a - b$.

- $a - b$ open circuited
- Turn off all independent sources

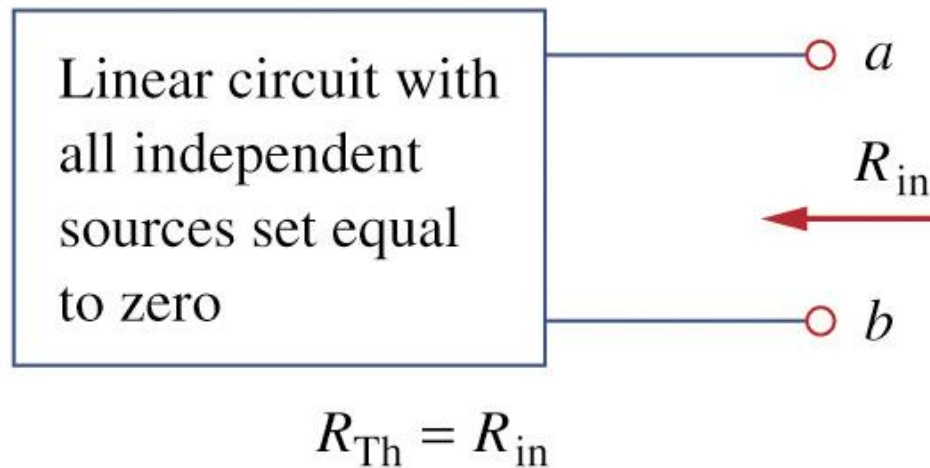


CASE 1




If the network has no dependent sources:

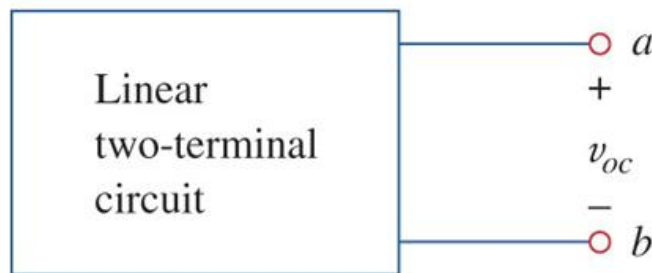- Turn off all independent source.
- R_{Th} : can be obtained via simplification of either parallel or series connection seen from a-b



$$V_{Th} = v_{oc}$$

(a)

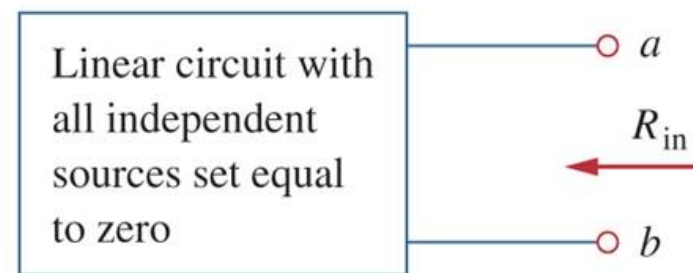

$$R_{Th} = R_{in}$$

(b)




CASE 2

- If the network has dependent sources
- Turn off all independent sources.
- Apply a voltage source v_o at a-b

$$R_{Th} = \frac{v_o}{i_o}$$

- Alternatively, apply a current source i_o at a-b

$$R_{Th} = \frac{v_o}{i_o}$$

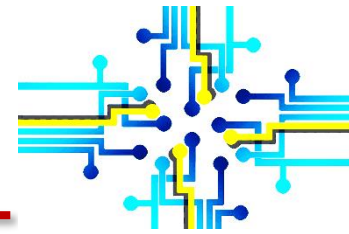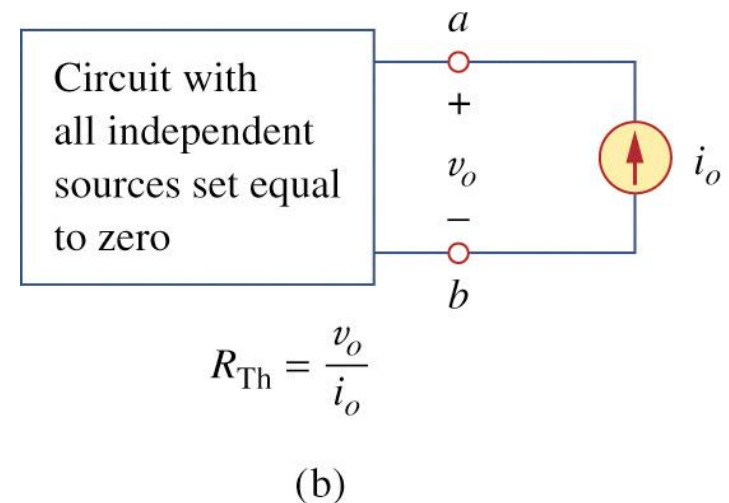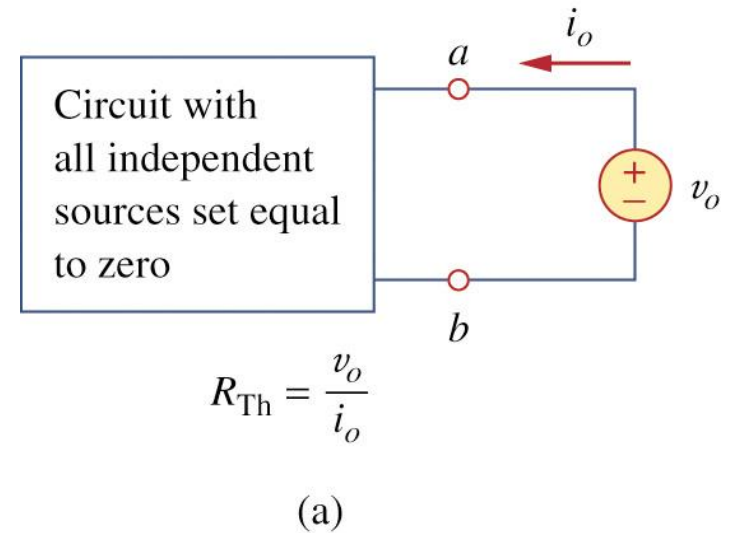


Thevenin's Theorem




- ❑ Thevenin's theorem is very powerful in circuit analysis.
- ❑ It allows one to simplify a circuit.
- ❑ A large circuit may be replaced by a single independent voltage source and a single resistor.
- ❑ The equivalent circuit behaves externally exactly the same as the original circuit.
- ❑ The Thevenin's resistance may be negative, indicating that the circuit has ability providing power

Example 6

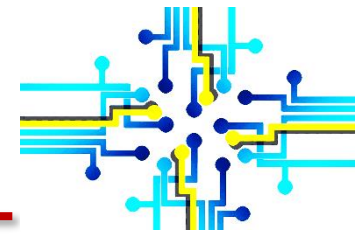

- Find the Thevenin's equivalent circuit of the circuit shown in Fig, to the left of the terminals a-b. Then find the current through $R_L = 6, 16, \text{ and } 36 \Omega$.

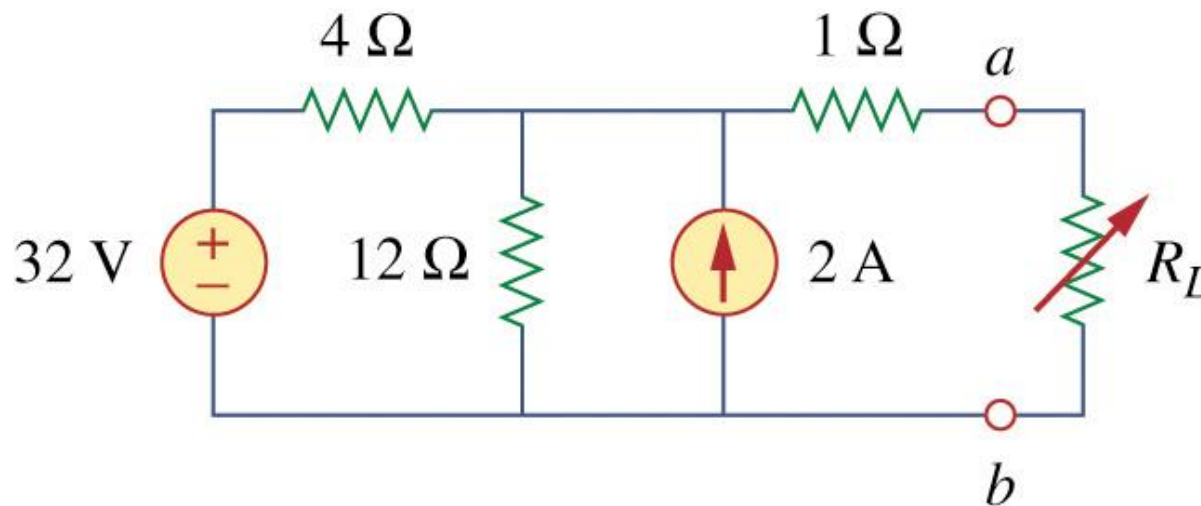


Example 6



□ Find R_{Th}


R_{Th} : 32V voltage source \rightarrow short
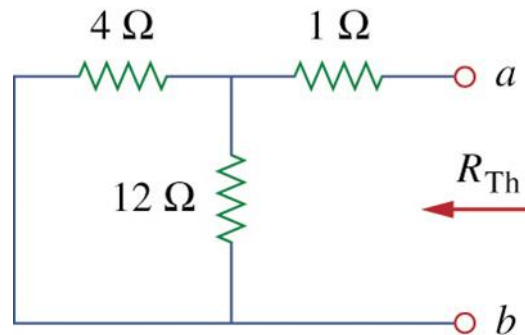
$$R_{Th} = 4 \parallel 12 + 1 = \frac{4 \times 12}{16} + 1 = 4\Omega$$



(a)

Example 6

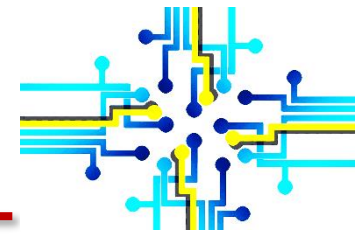

□ Find V_{Th}

(1) *Mesh analysis*

$$-32 + 4i_1 + 12(i_1 - i_2) = 0, \quad i_2 = -2A$$


$$\therefore i_1 = 0.5A$$

$$V_{Th} = 12(i_1 - i_2) = 12(0.5 + 2.0) = 30V$$

(2) Alternatively, Nodal Analysis

$$(32 - V_{Th}) / 4 + 2 = V_{Th} / 12$$

$$\therefore V_{Th} = 30V$$

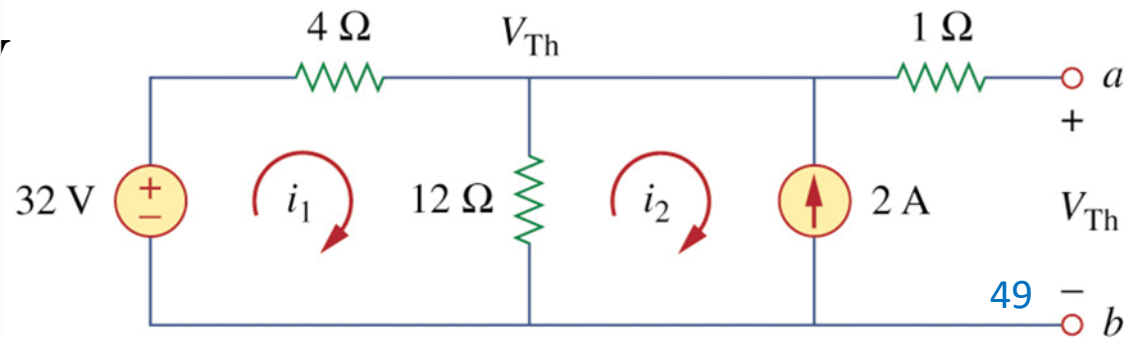


(b)

Find I_L



To get i_L :
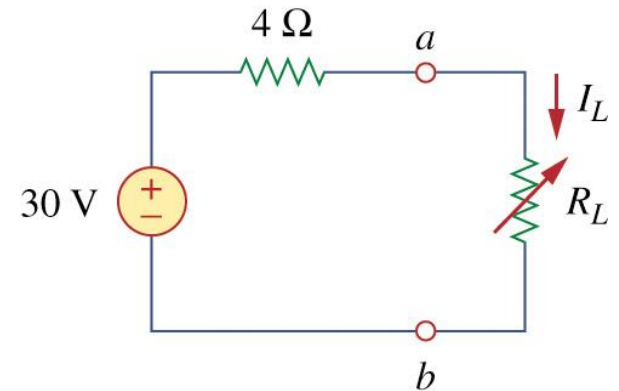
$$i_L = \frac{V_{Th}}{R_{Th} + R_L} = \frac{30}{4 + R_L}$$



$$R_L = 6 \rightarrow I_L = 30/10 = 3A$$


$$R_L = 16 \rightarrow I_L = 30/20 = 1.5A$$

$$R_L = 36 \rightarrow I_L = 30/40 = 0.75A$$


Norton's Theorem



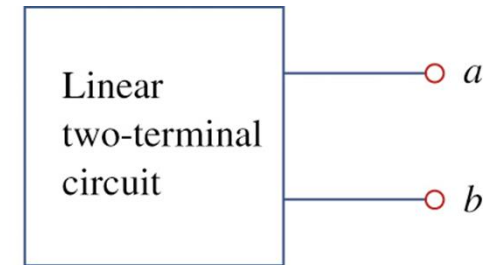
- Similar to Thevenin's theorem, Norton's theorem states that a linear two terminal circuit may be replaced with an equivalent circuit containing a resistor and a current source.
- The Norton resistance will be exactly the same as the Thevenin.




(a)

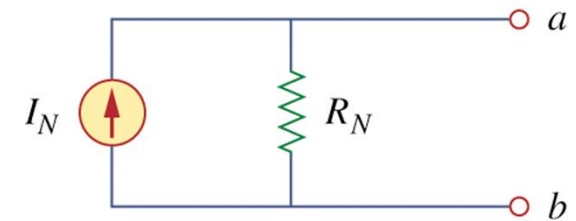

(b)

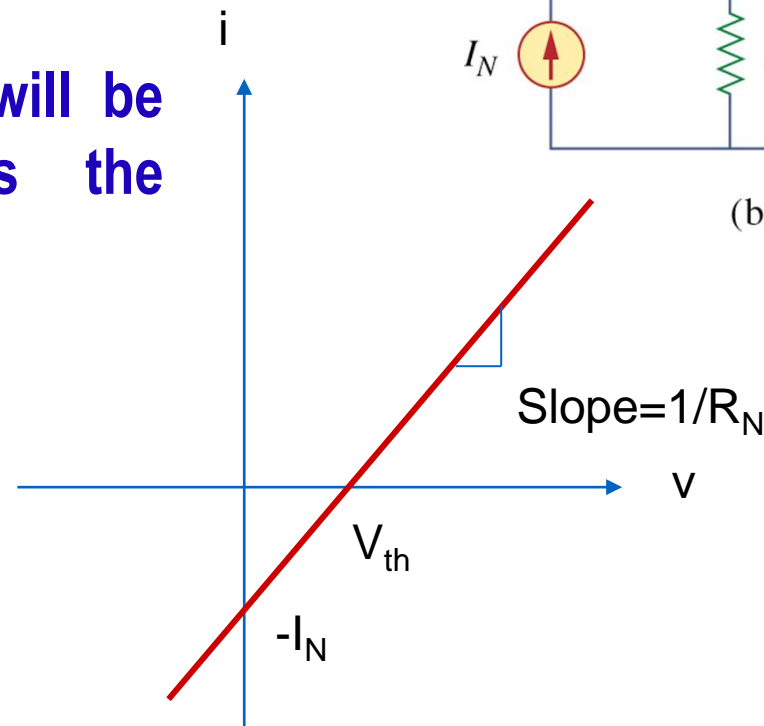

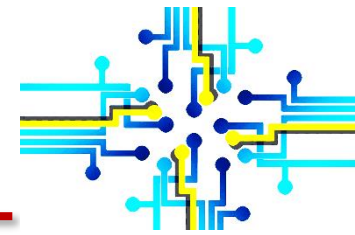


How to Find Norton Current

- Thevenin and Norton resistances are equal:

$$R_N = R_{Th}$$

- Short circuit current from a to b :

$$I_N = i_{sc} = \frac{V_{Th}}{R_{Th}}$$

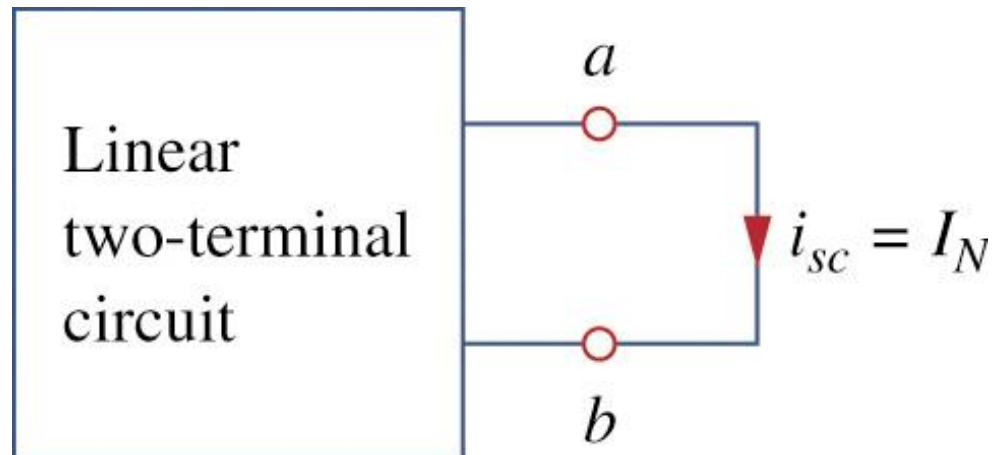

Thevenin or Norton equivalent circuit :




- The open circuit voltage v_{oc} across terminals a and b
- The short circuit current i_{sc} at terminals a and b
- The equivalent or input resistance R_{in} at terminals a and b when all independent source are turn off.

$$V_{Th} = v_{oc}$$


$$I_N = i_{sc}$$

$$R_{Th} = \frac{V_{Th}}{I_N} = R_N$$

Example 7

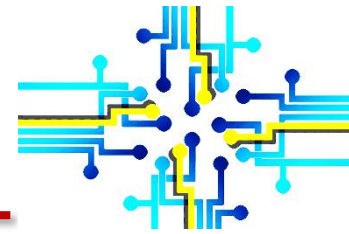

- Find the Norton equivalent circuit of the circuit in Fig.

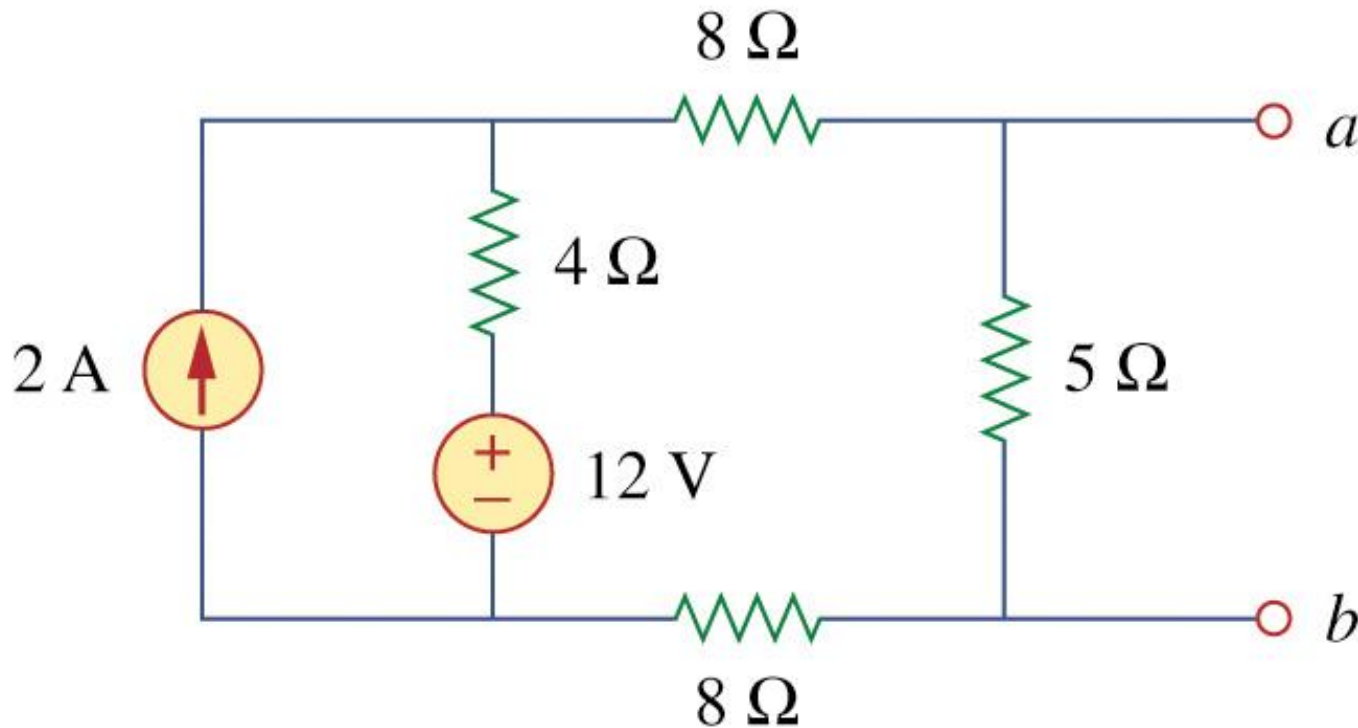

Example 7




□ Determine the Thevenin or Norton equivalent circuit requires that we find:

- The open-circuit voltage across terminals a and b.
- The short-circuit current at terminals a and b.
- The equivalent or input resistance at terminals a and b when
- all independent sources are turned off.

To find R_N
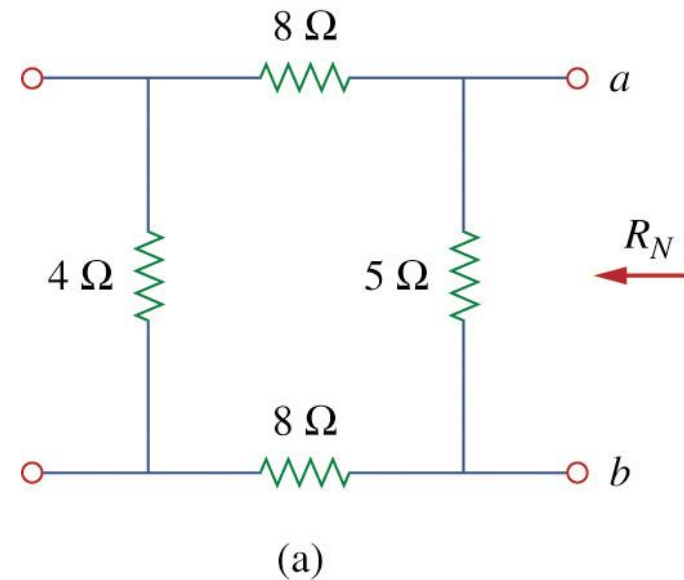
$$\begin{aligned} R_N &= 5 \parallel (8 + 4 + 8) \\ &= 5 \parallel 20 = \frac{20 \times 5}{25} = 4\Omega \end{aligned}$$



To Find I_N




□ To find we short-circuit terminals **a** and **b**, as shown in Fig.

□ We ignore the resistor **5Ω** because it has been short-circuited

short – circuit terminals a and b .

$$\text{Mesh : } i_1 = 2A, \quad 20i_2 - 4i_1 - 12 = 0$$

$$i_2 = 1A = i_{sc} = I_N$$

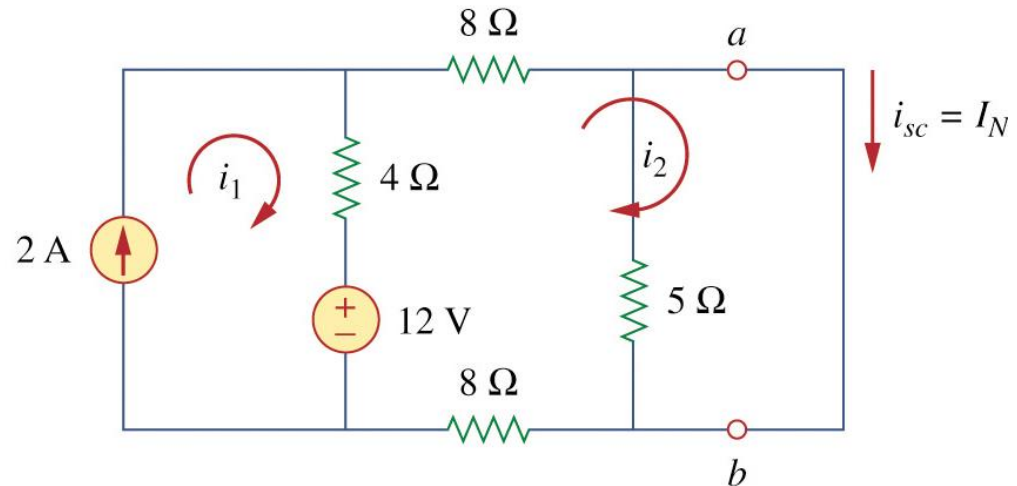

(b)

Alternative Method for I_N



$$I_N = \frac{V_{Th}}{R_{Th}}$$

V_{Th} : open – circuit voltage across terminals a and b

Mesh analysis:

$$i_3 = 2A, \quad 25i_4 - 4i_3 - 12 = 0$$

$$\therefore i_4 = 0.8A$$

$$\therefore v_{oc} = V_{Th} = 5i_4 = 4V$$

